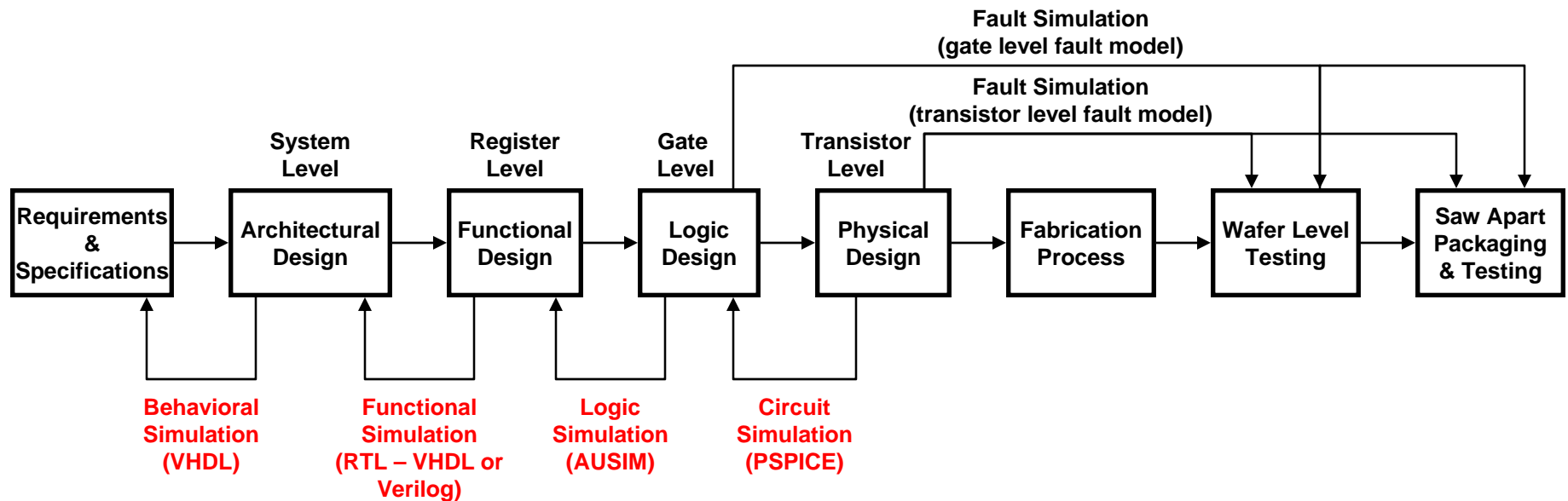


Example of Digital System Design

- The integrated circuit design process



- Note all the simulation (design verification) - helps to ensure the design works and assists in debugging design errors
- In order to simulate a circuit, we must describe it in a manner that can be interpreted and understood by the simulator.


Design Capture with Hardware Description Languages

- Netlist
 - Connections via signal name (like ASL)
- Schematic
 - Connections either explicit or via signal name
 - Produces a netlist for simulation
- Higher level language (VHDL or Verilog)
 - Synthesis to gate level netlist
- All of these design descriptions can go to simulation for design verification

Key Ingredients of Hardware Description Languages (HDLs)

- Circuit statement:

- Circuit name
- Inputs
- Outputs

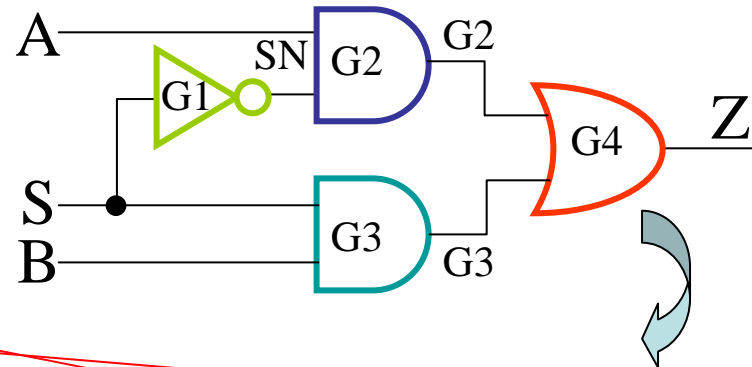

- Component statements:


- Component type
- Component instantiation
- Inputs signals
- Output signals

```

ckt: MUX in: A B S out: Z ;
not: G1 in: S out: SN ;
and: G2 in: A SN out: G2 ;
and: G3 in: S B out: G3 ;
or: G4 in: G2 G3 out: Z ;
  
```


Hierarchical Design

 - Hierarchical design saves time & design errors
 - Once a subcircuit has been simulated & is known to work
 - Most HDLs support hierarchical design



Key Ingredients of HDLs

 - Hierarchy (subcircuits)
- Connection via signal names (or netnames)



- Keyword notation
- Positional notation
- Bus notation

```


subckt: MUX in: A B S out: Z ;
not: G1 in: S out: SN ;
and: G2 in: A SN out: G2 ;
and: G3 in: S B out: G3 ;
or: G4 in: G2 G3 out: Z ;
ckt: MUX4 in: In[0:3] S[0:1] out: Out ;
MUX: M1 in: In0 In1 S0 out: M1 ;
MUX: M2 in: In2 In3 S0 out: M2 ;
MUX: M3 in: M1 M2 S1 out: Out ;
    
```

Hierarchical Design

- Hierarchical design supported in most HDLs
 - VHDL, Verilog, ASL


Netlist
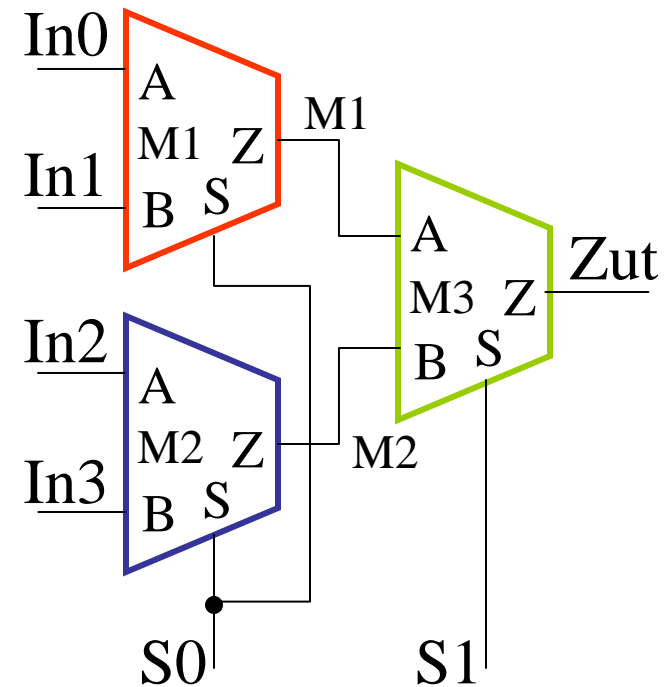
```
subckt: MUX in: A B S out: Z ;
not: G1 in: S out: SN ;
and: G2 in: A SN out: G2 ;
and: G3 in: S B out: G3 ;
or: G4 in: G2 G3 out: Z ;
ckt: MUX4 in: In[0:3] S[0:1]
      out: Zut ;
MUX: M1 in: In0 In1 S0 out: M1 ;
MUX: M2 in: In2 In3 S0 out: M2 ;
MUX: M3 in: M1 M2 S1 out: Out ;
```



Design Verification


Schematic (or logic diagram)

 

Netlist

```
ckt: MUX in: A B S out: Z ;  
not: G1 in: S out: SN ;  
and: G2 in: A SN out: G2 ;  
and: G3 in: S B out: G3 ;  
or: G4 in: G2 G3 out: Z ;
```

Logic Simulation

 

Design Verification

- Logic simulation results used
 - To verify proper operation of design
 - To find and fix problems (errors) in design
 - aka *debugging*

<i>Input Stimuli</i> (or vectors)			<i>Simulation</i> <i>Results</i>		
#	ABS	;	#	ABS	Z ;
	000			000	0
	001			001	0
	010			010	0
	011			011	1
	100			100	1
	101			101	0
	110			110	1
	111			111	1

compare simulation results to truth table

Key Ingredients of Logic Design


- Logic simulation results used
 - To verify proper operation of design (design verification)
 - To find and fix problems (errors) in design (aka *debugging*)

<i>Input Stimuli</i> (or vectors)			<i>Simulation</i> <i>Results</i>		
#	ABS	;	#	ABS	Z ;
	000			000	0
	001			001	0
	010			010	0
	011			011	1
	100			100	1
	101			101	0
	110			110	1
	111			111	1

Simulation

Design Capture Input

Schematic diagram

 


Netlist

```

ckt: MUX in: A B S out: Z ;
not: G1 in: S out: SN ;
and: G2 in: A SN out: G2 ;
and: G3 in: S B out: G3 ;
or: G4 in: G2 G3 out: Z ;
    
```

Computer Emulation

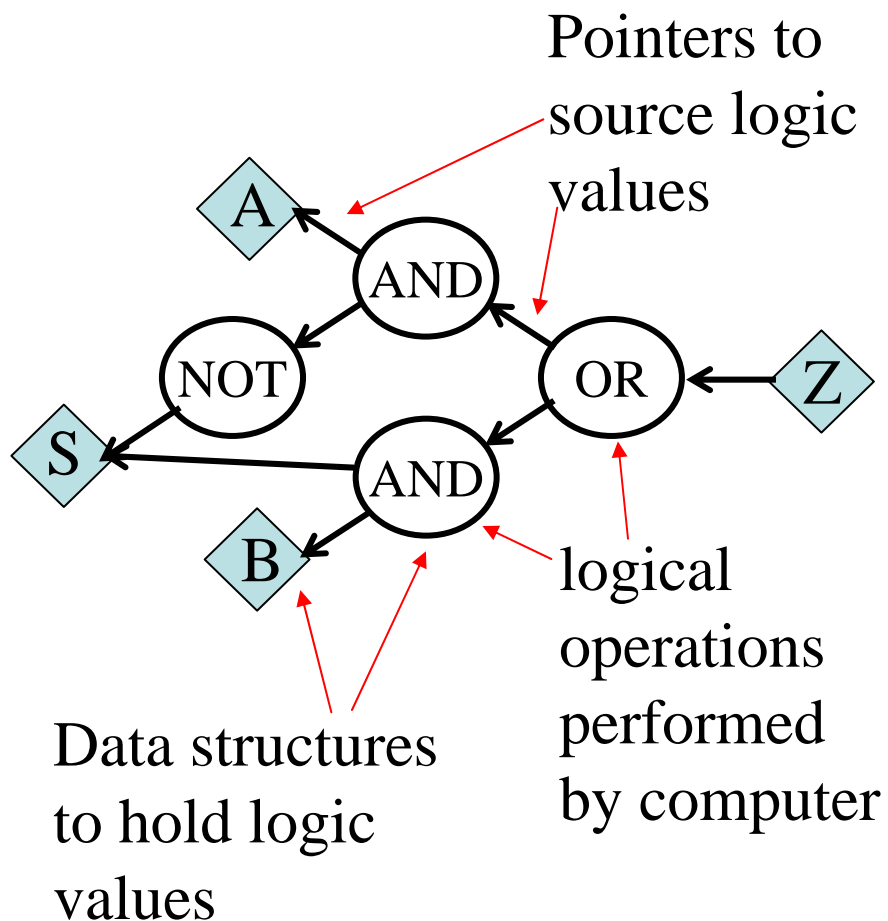

Types of Simulators

- Compiled Simulator (AUSIM)
 - Simulation continues until circuit is stable
 - No changing logic values within circuit
 - Aka: unit delay or logic simulator
 - All gates in circuit have a finite unit delay
 - Good for initial design verification
 - Short simulation times
- Event-Driven Simulator
 - Simulation events scheduled in time
 - Circuit may not be stable when input changes
 - Aka: timing simulator
 - Gates have real delays base on intrinsic & extrinsic factors
 - More accurate for real circuits
 - longer simulation times and more computer intensive

Other CAD Tools in Logic Design

- Audits for potential design problems
 - Such as “no-connects” or multiple gates driving same net
 - Usually part of another tool (schematic capture or simulator)
- Logic minimization tools
 - Handles combinational logic circuits too big for K-maps
- Timing analysis
 - Finds and reports worst case timing delay path
 - Like P_{del} but uses actual timing parameters per gate