

Instantaneous Power

Instantaneous power (in watts) : the power at any instant of time

$$p(t) = v(t) \times i(t)$$

Where:

$$v(t) = V_m \cos(\omega t + \theta_v)$$


$$i(t) = I_m \cos(\omega t + \theta_i)$$

$$p(t) = \frac{V_m I_m}{2} \{ \cos(\theta_v - \theta_i) + \cos(2\omega t + \theta_v + \theta_i) \}$$



Instantaneous Power

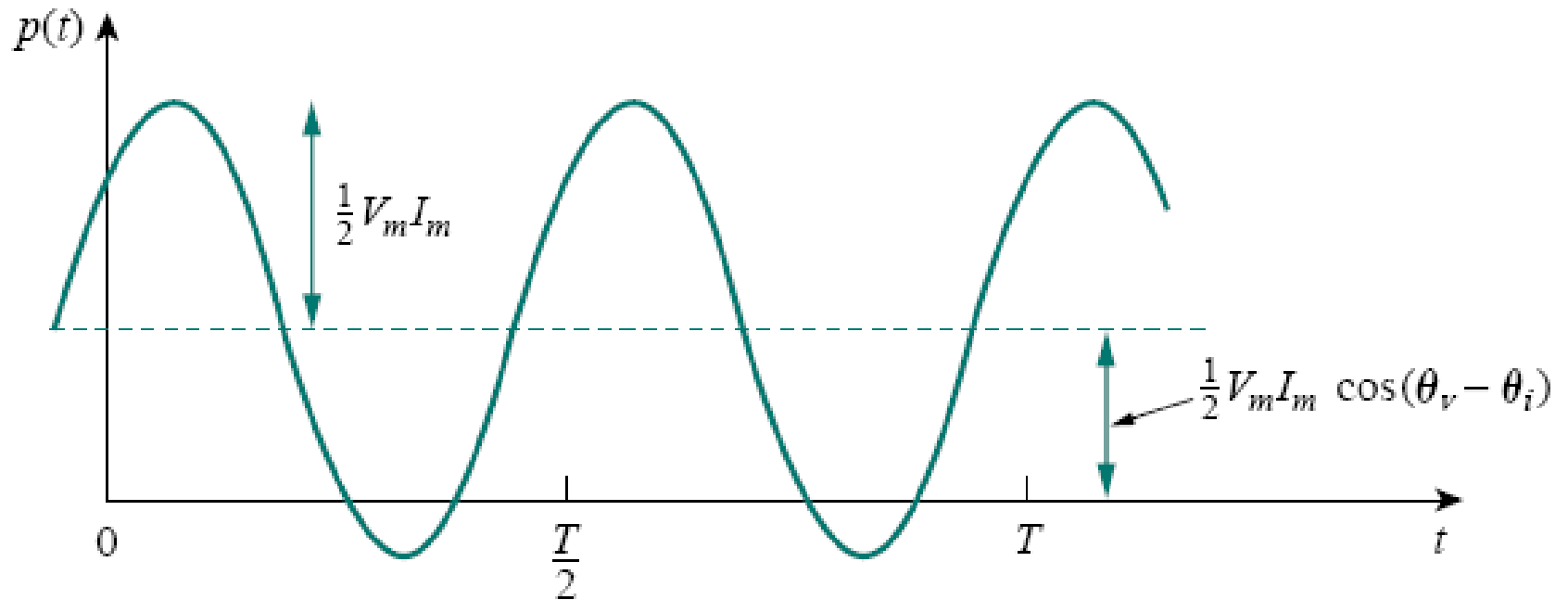The instantaneous power $p(t)$ entering a circuit



Average Power

Average Power (in watts) : the average of the instantaneous power over one period

$$P = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i)$$

$$P = \frac{V_m I_m}{2} \cos \theta$$

Where:

$$\theta = \theta_v - \theta_i$$



Average Power

$$P = V_{\text{eff}} I_{\text{eff}} \cos \theta$$

$$V_{\text{rms}} \text{ or } V_{\text{eff}} = \frac{V_m}{\sqrt{2}}$$

$$I_{\text{rms}} \text{ or } I_{\text{eff}} = \frac{I_m}{\sqrt{2}}$$



Circuit Elements

(a) Resistors:

In purely resistive circuit, v and i are in phase.
 $\theta_v = \theta_i$. Therefore $\theta = 0$.

$$P = \frac{V_m I_m}{2} \cos 0^\circ = \frac{V_m I_m}{2} = V_{\text{eff}} I_{\text{eff}} = \frac{V_{\text{eff}}^2}{R} = (I_{\text{eff}})^2 R$$

The average power is only dissipated in a purely resistive circuit. For a purely inductive and capacitive, the average power is zero.



Circuit Elements

(b) Inductors:

In purely inductive circuit, v leads by 90° ,
therefore $\theta = 90^\circ$

$$P = \frac{V_m I_m}{2} \cos(90^\circ) = 0$$

(c) Capacitors:


In purely capacitive circuit, I leads by 90° ,
therefore $\theta = -90^\circ$

$$P = \frac{V_m I_m}{2} \cos(-90^\circ) = 0$$



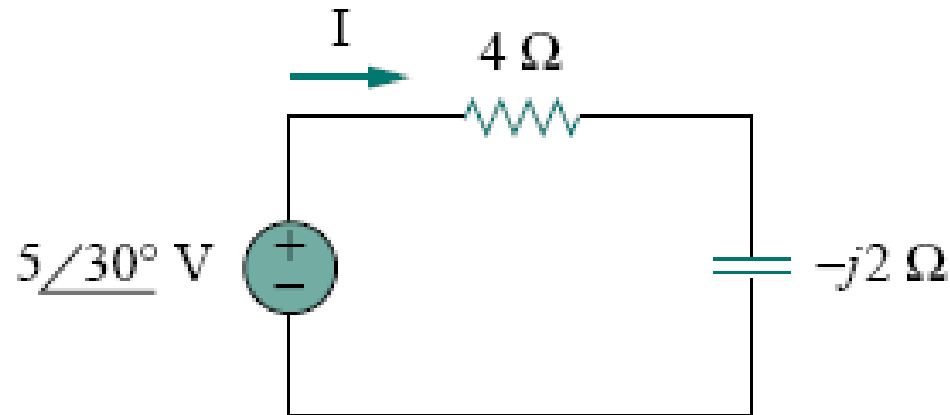Example 2

Find the average power supplies by the source and the average power absorbed by the resistor.




Reference : Alexander, Sadiku Chapter 11 - page 462



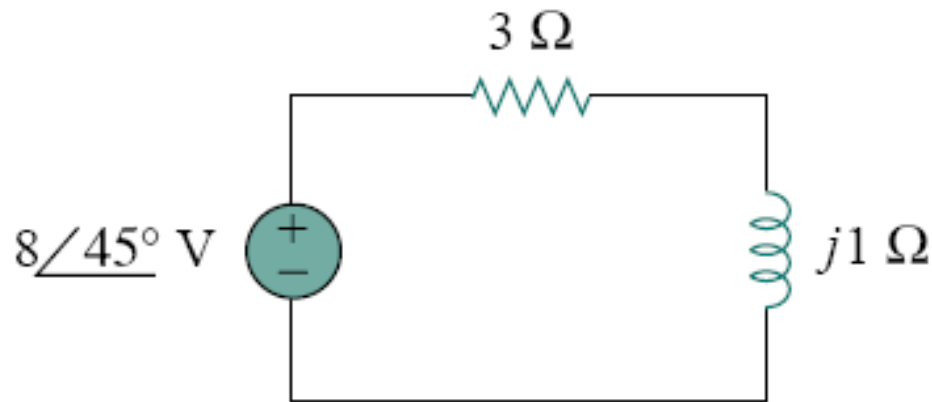Exercise 2

Calculate the average power absorbed by the resistor and inductor. Find the average power supplies by the voltage source.



$$P_R = 9.6\text{W}$$

$$P_L = 0\text{W}$$

$$P = 9.6\text{W}$$

