



Faculty of Industrial Technology

Suan Sunandha Rajabhat University

Software and Systems Engineering



CPE3202

Pornpawit Boonsrimuang




Combinational Logic Circuits

- Implementation of Logic Diagrams from Boolean Expressions
- Using NAND and NOR gates
- Using NAND and NOR gates for the inversion operation
- Implementation of DeMorgan's theorem
- Implementation of the XOR
- Implementation of the XOR function with NAND gate only
- Implementation of the Boolean expression


Implementation of the Boolean expression

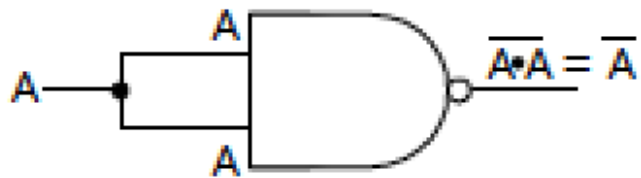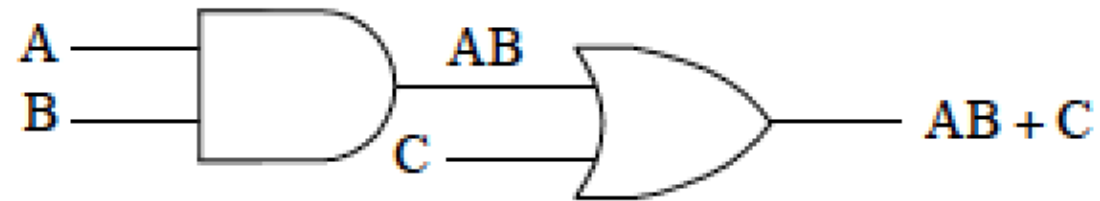


Implementation of DeMorgan's theorem

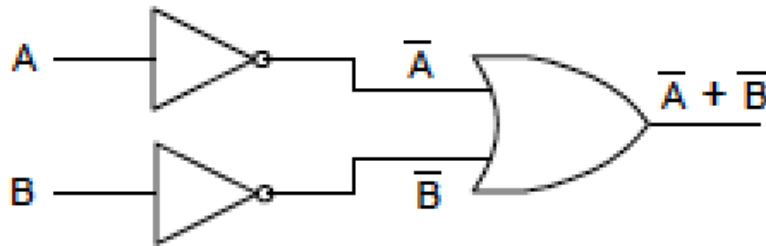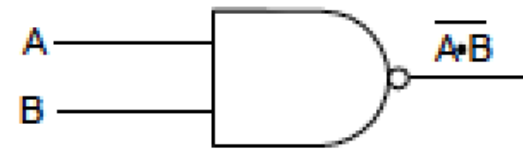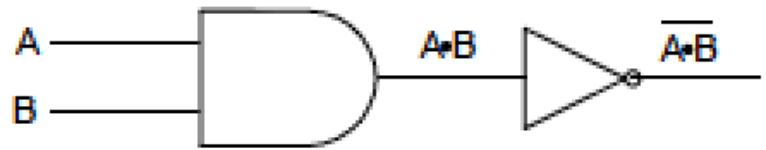

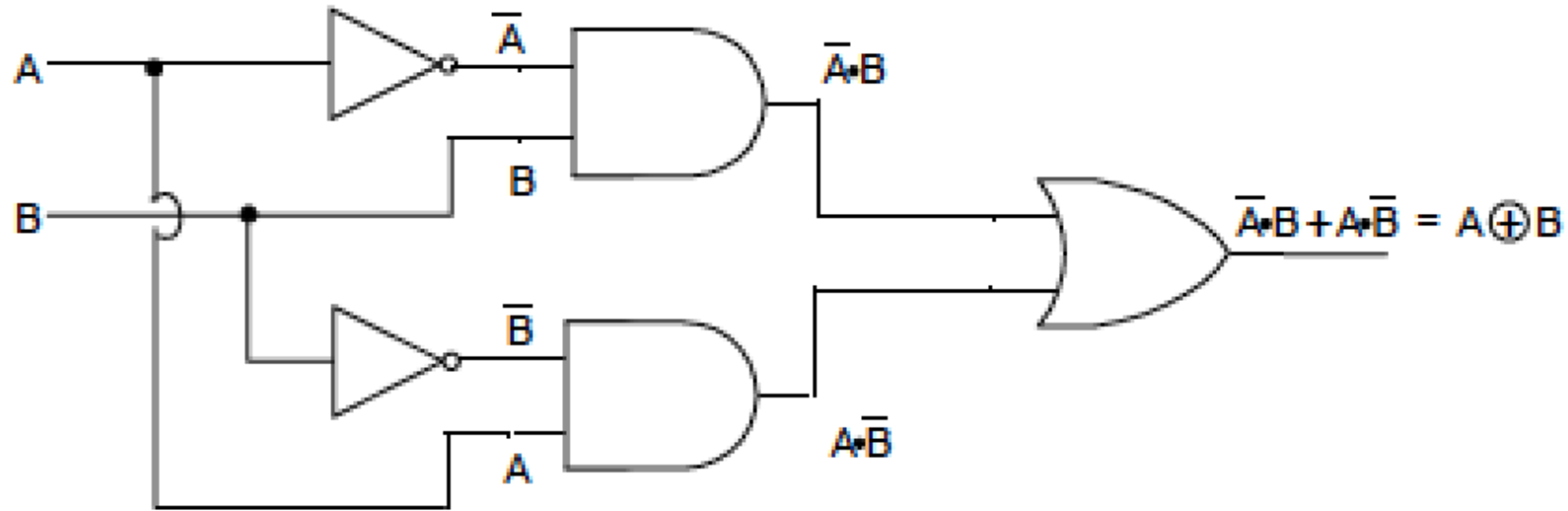
Implementation of the XOR function with AND gates




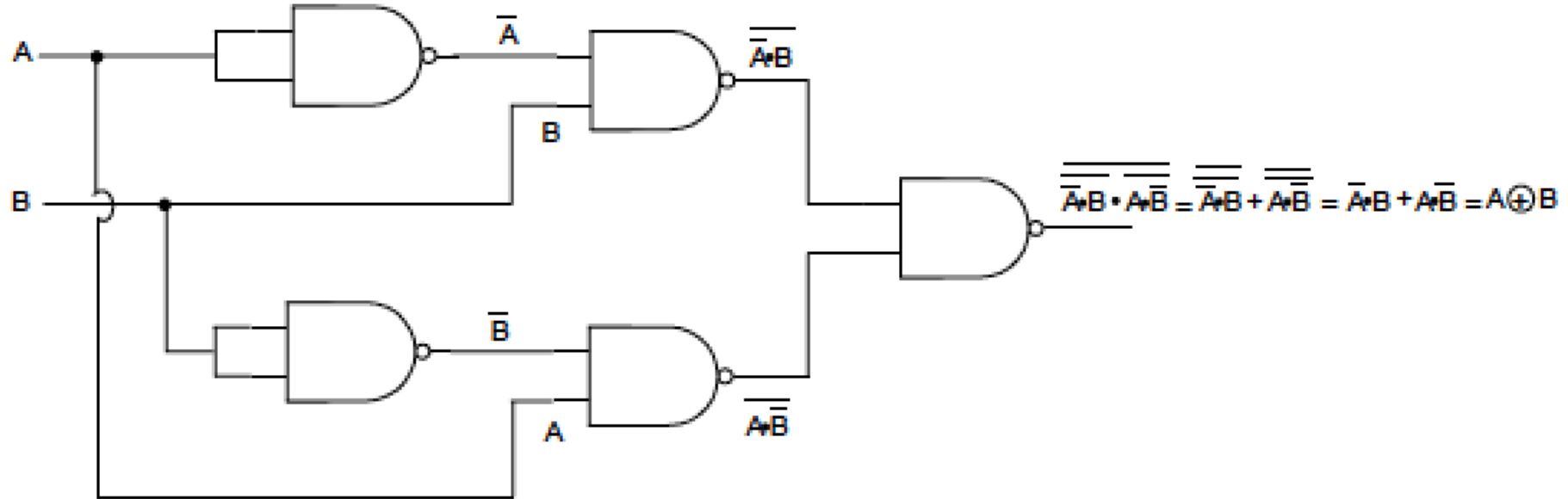
Implementation of the XOR function with NAND gates only





Implementation of the Boolean expression

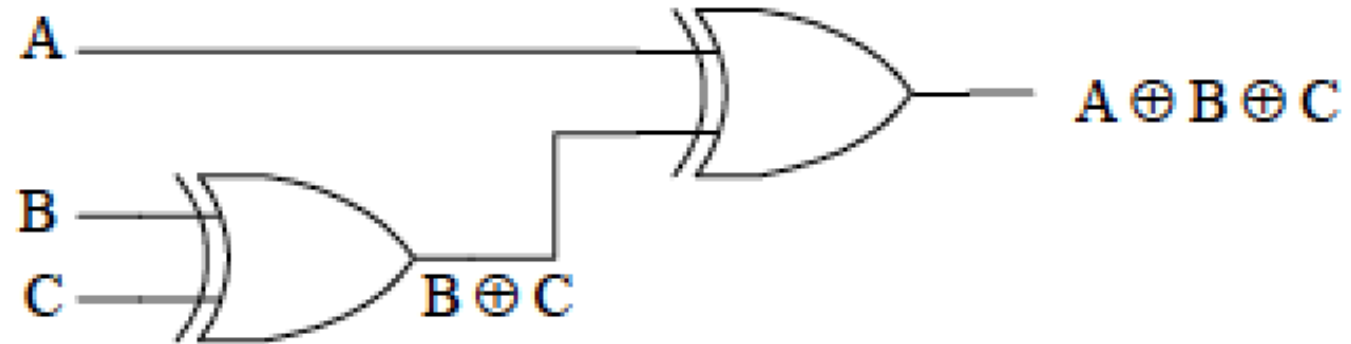



Implementation of the OR operation

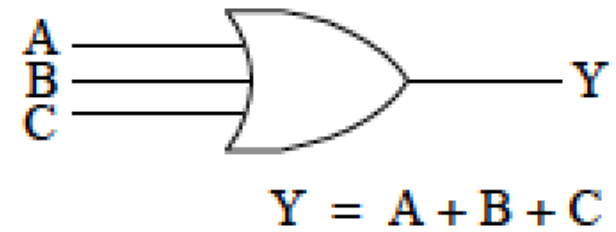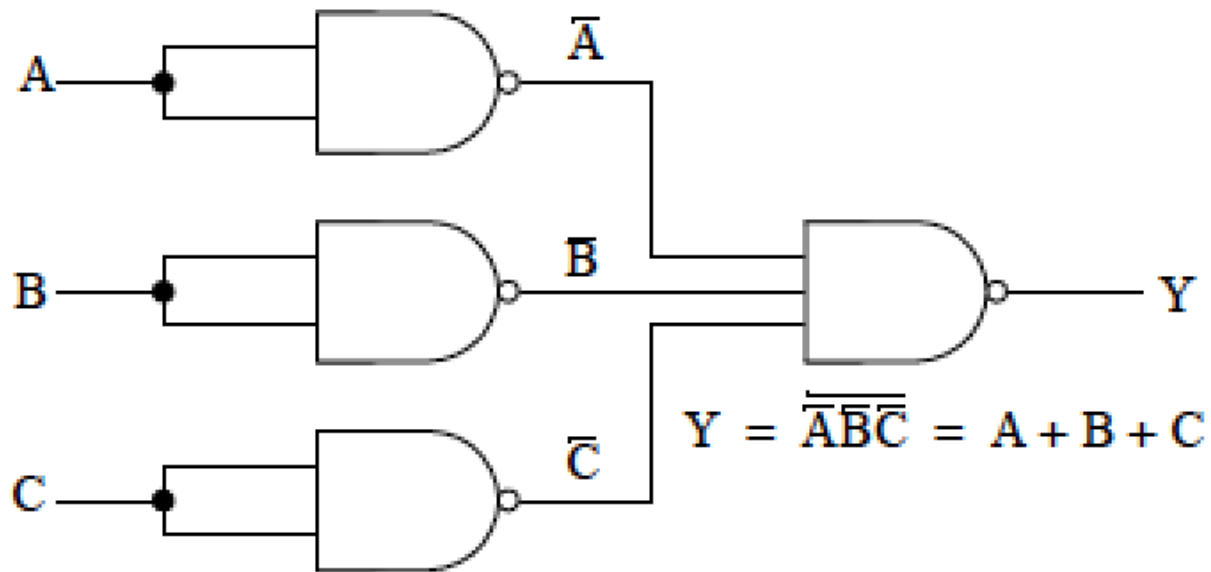


Implementation of the AND operation

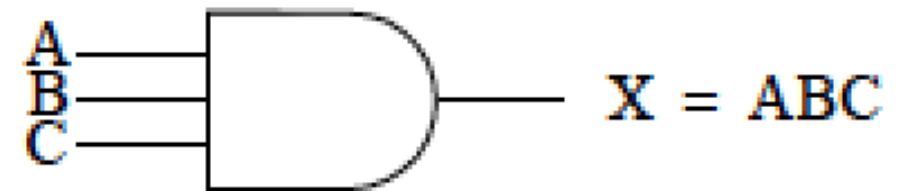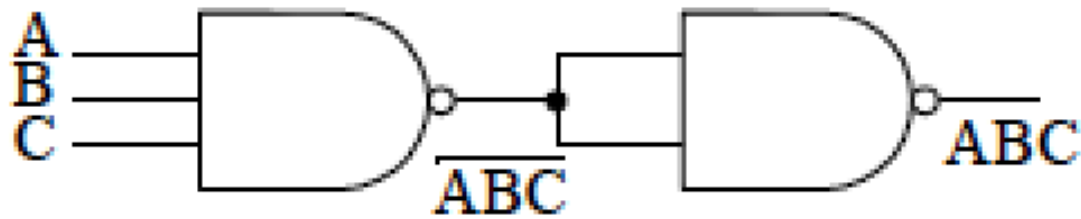


Implementation of the AND & NOR

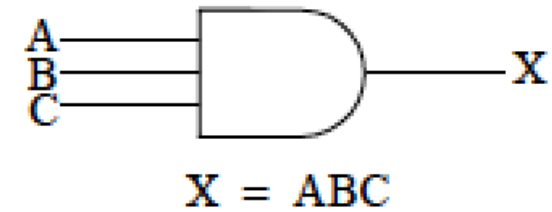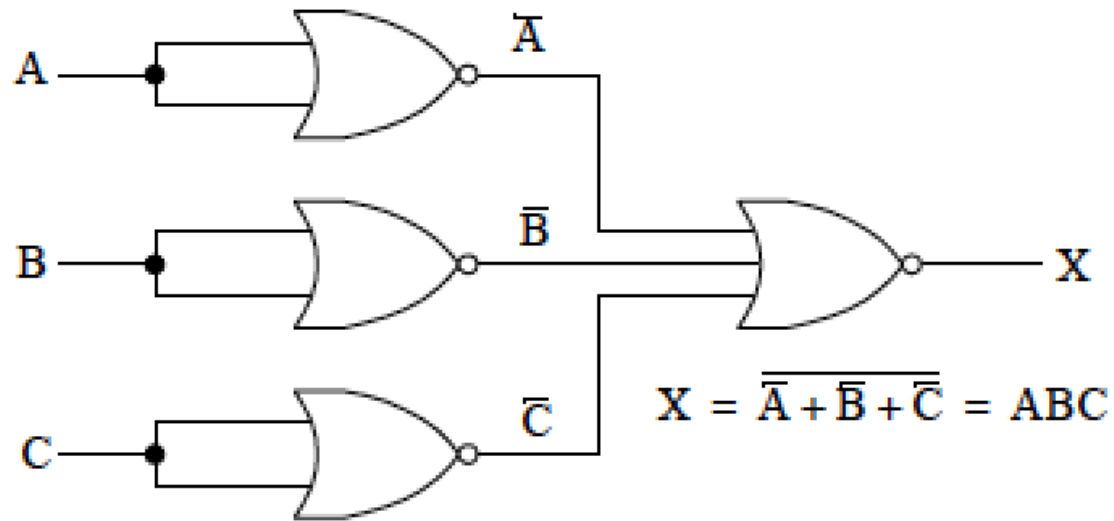


Implementation of the OR & NOR

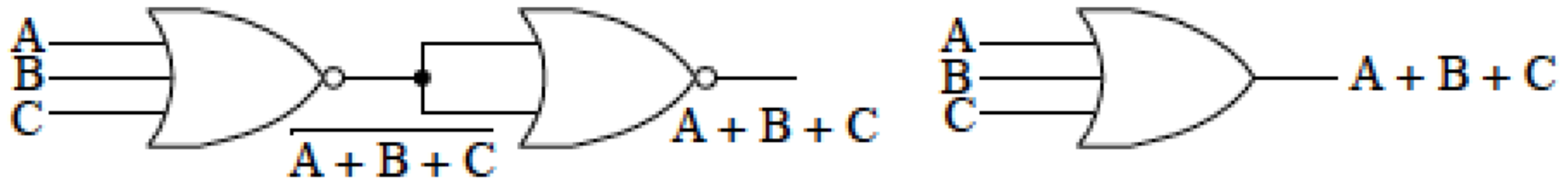


Implementation of the AND OR & Inverters

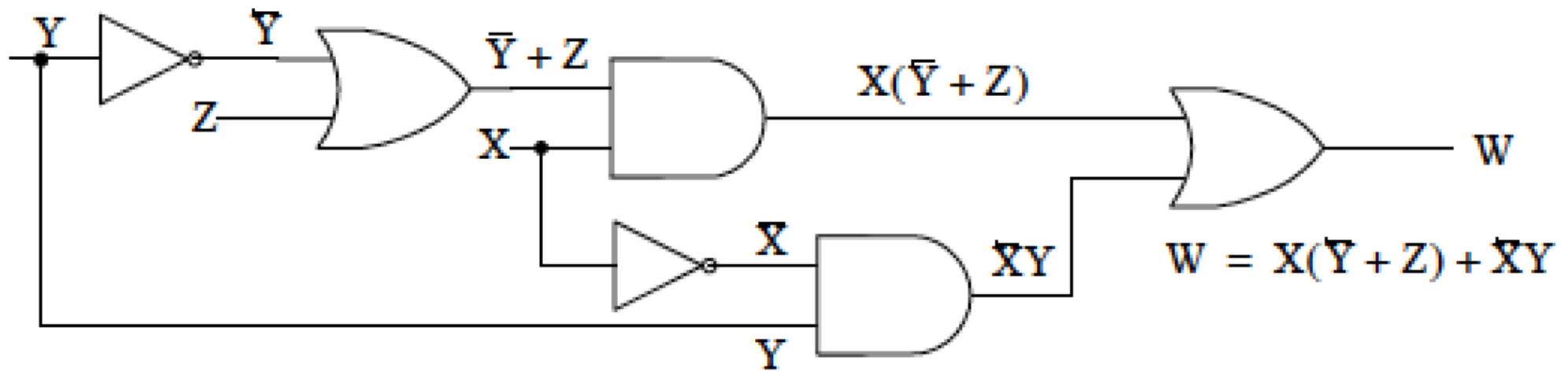

Implementation of the NAND gates

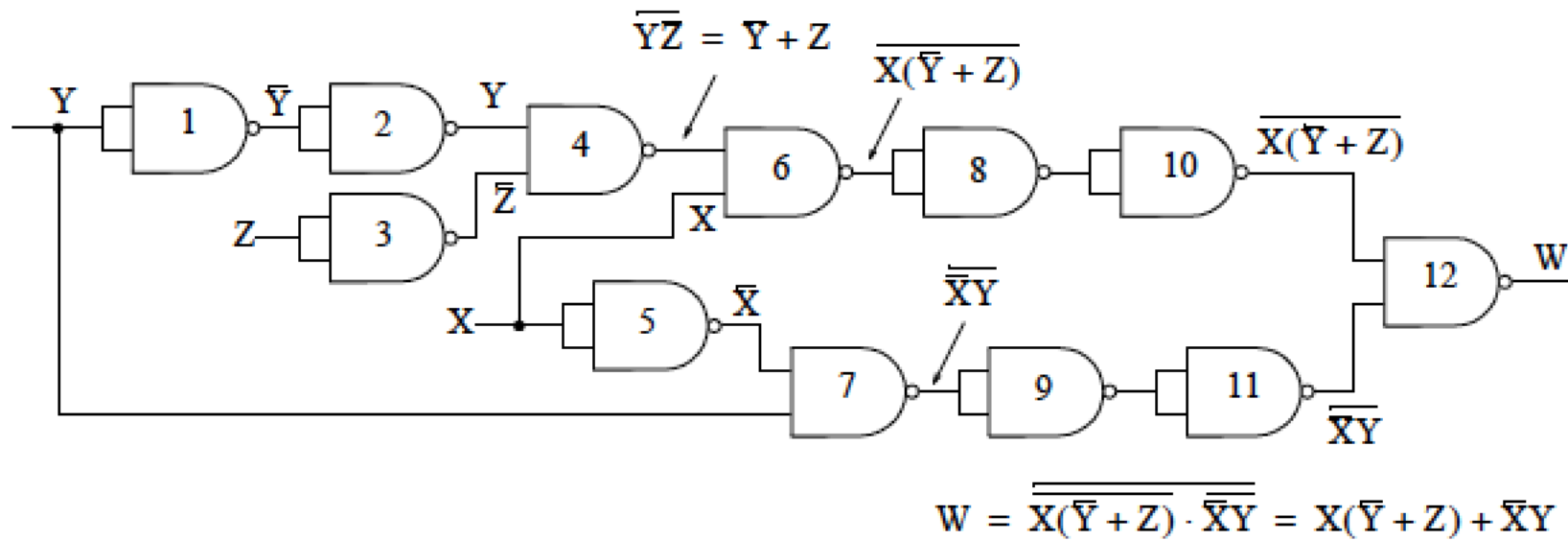


Implementation of the NAND

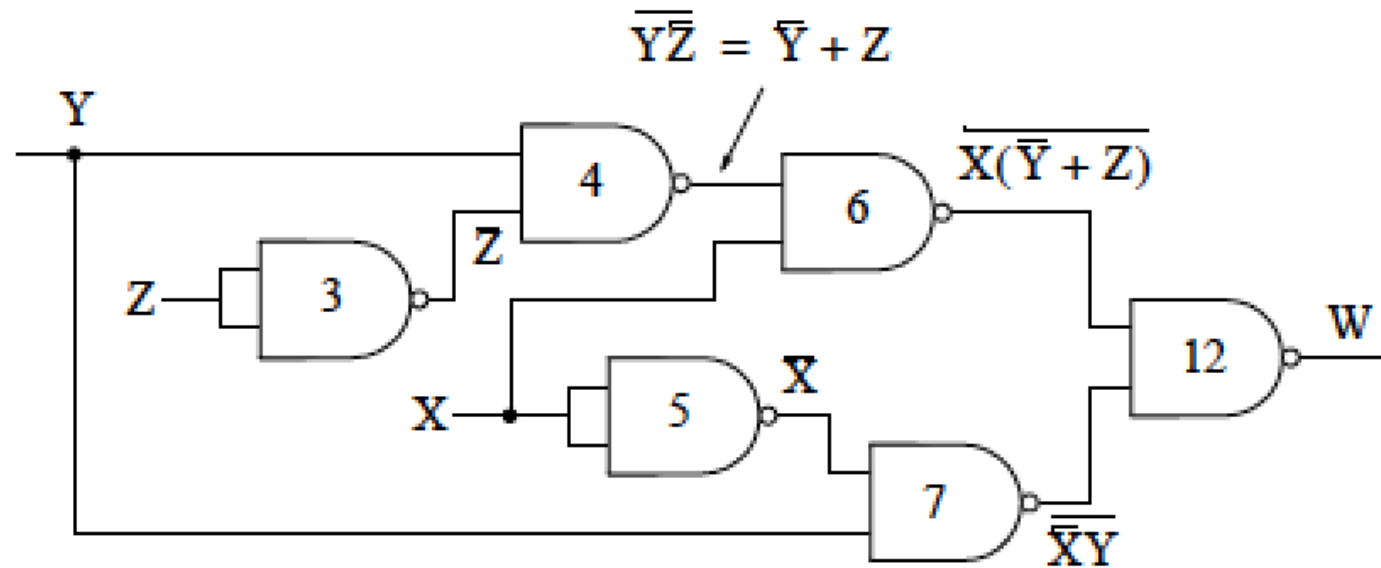


$$W = \overline{\overline{X(\bar{Y} + Z)} \cdot \overline{\bar{X}Y}} = X(\bar{Y} + Z) + \bar{X}Y$$


Implementation of the AND OR & Inverters

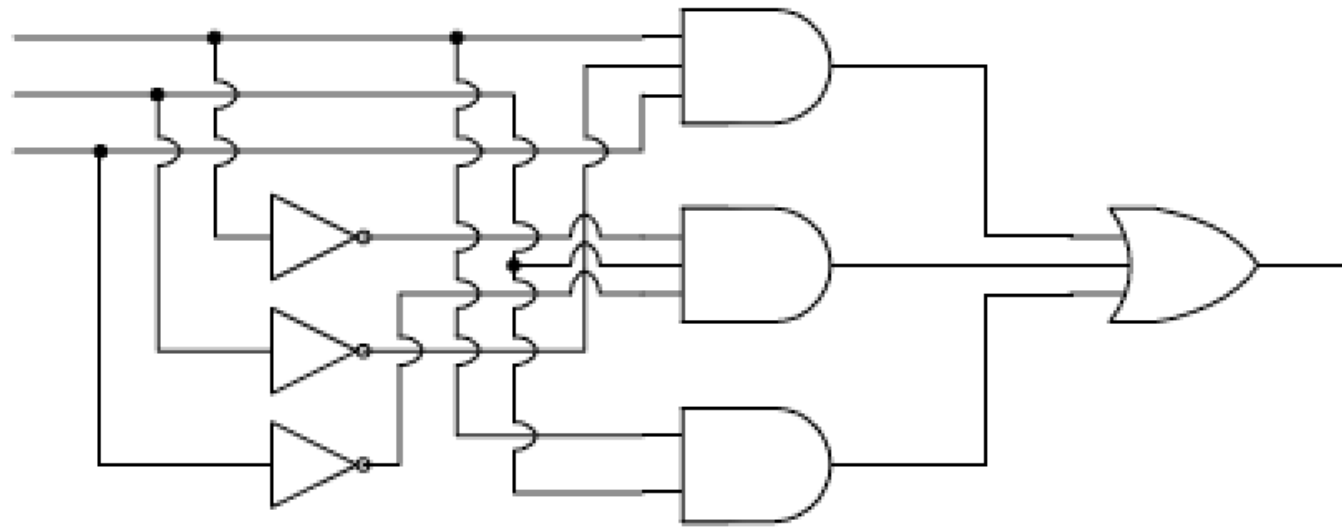

Implementation of NOR - unsimplified

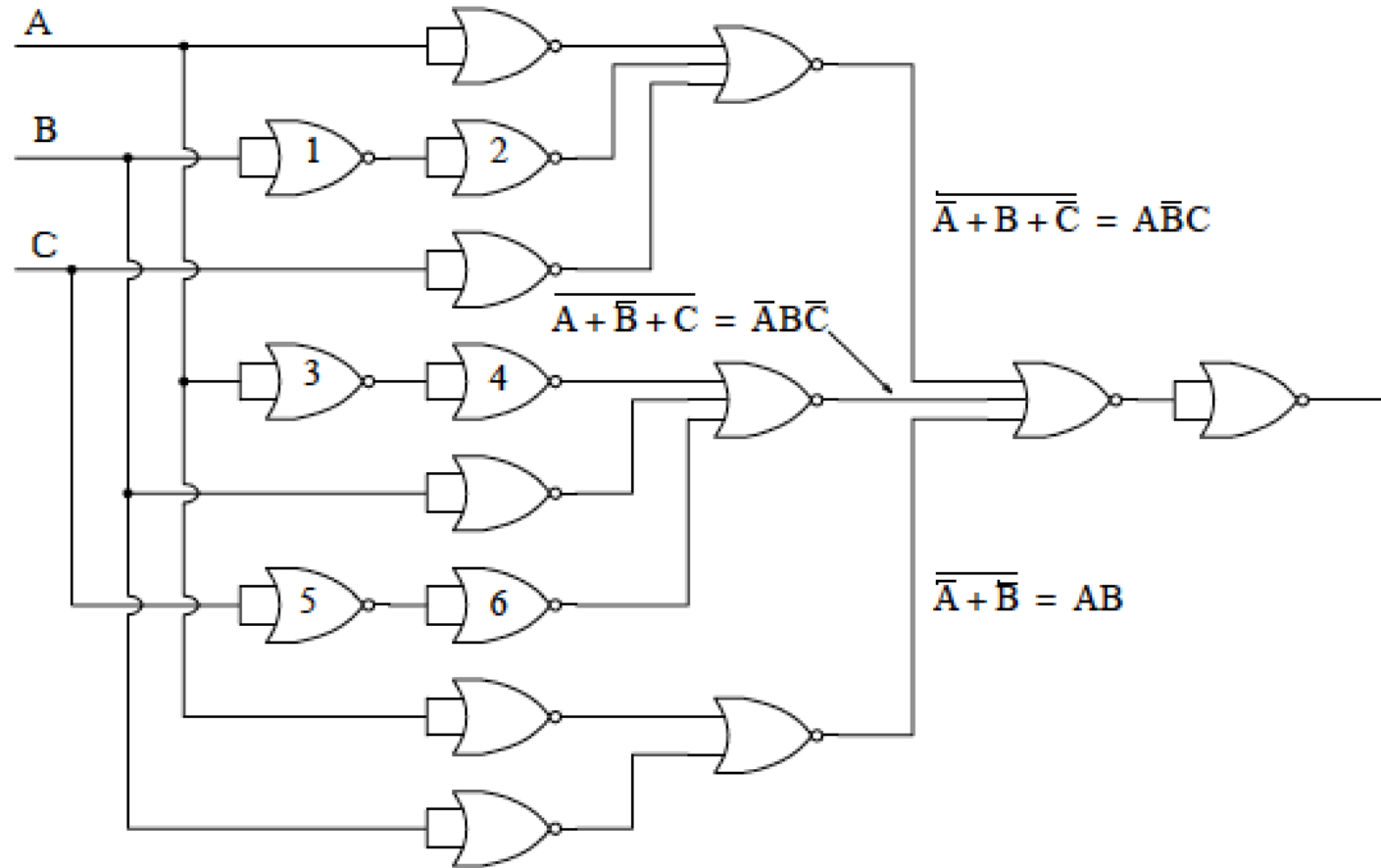

Implementation of NOR - simplified

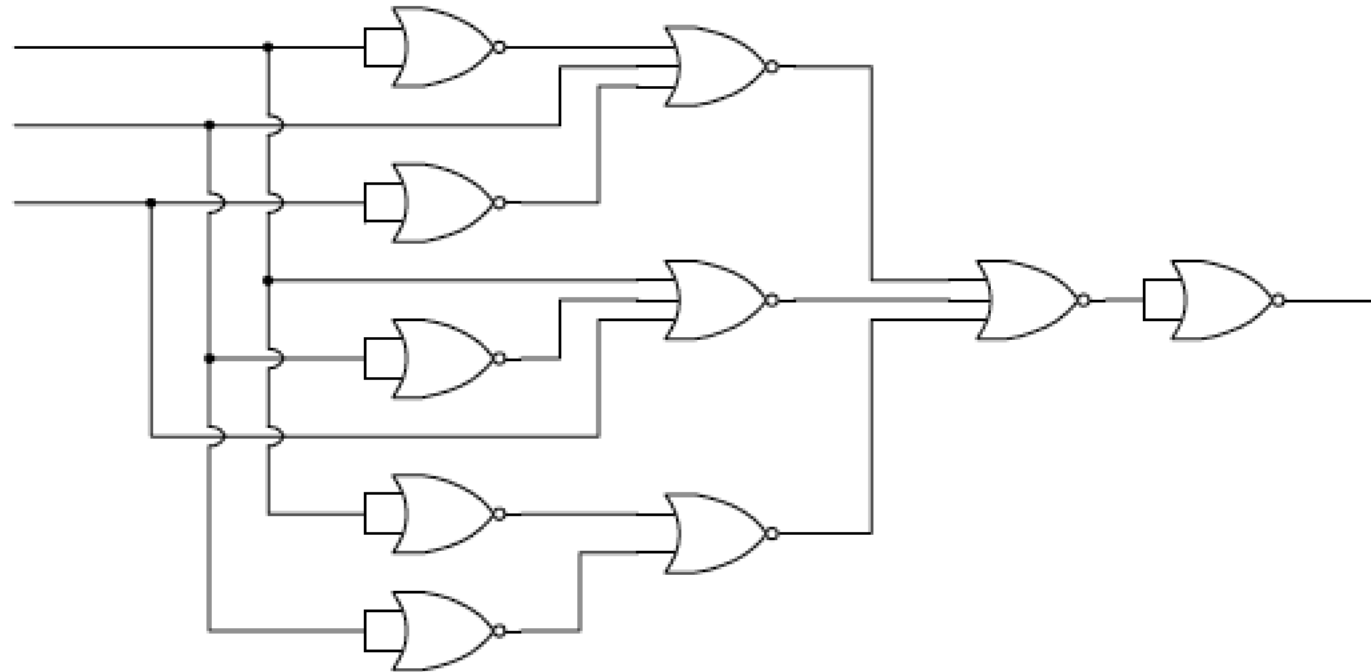


Ex.

$$D = \bar{A}BC + A\bar{B}C + ABC + B\bar{C}.$$


$$\begin{aligned} D &= \bar{A}BC + ABC + A\bar{B}C + ABC + B\bar{C} \\ &= BC(A + \bar{A}) + AC(B + \bar{B}) + B\bar{C} \\ &= BC + AC + B\bar{C} \\ &= B(C + \bar{C}) + AC \\ &= B + AC \end{aligned}$$




Output of the gates of logic

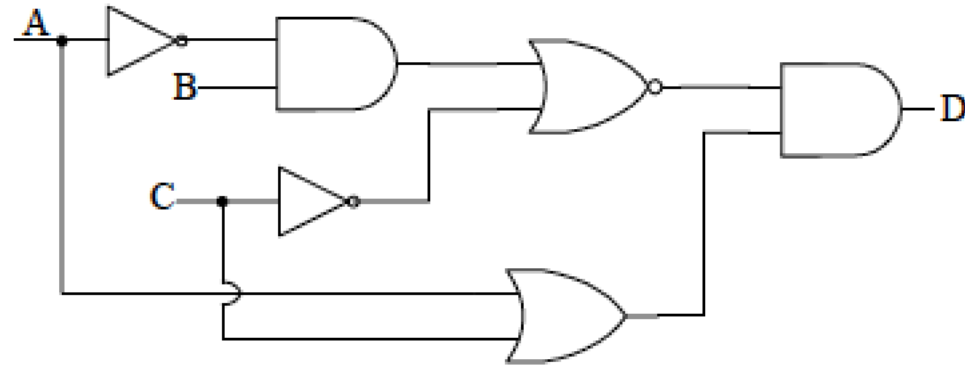


Ex.

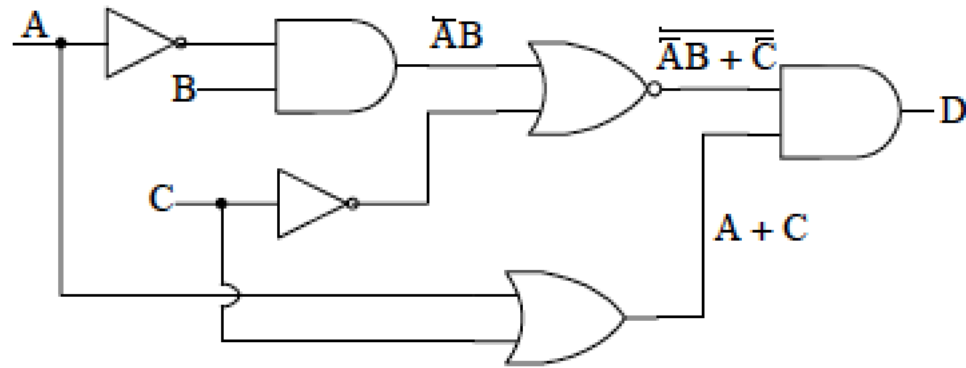

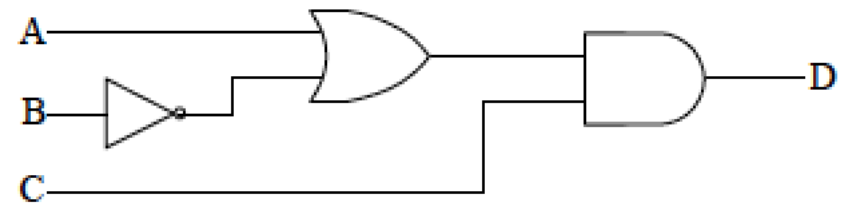
$$\begin{aligned} D &= (\overline{AB + \bar{C}})(A + C) = (\overline{A\bar{B}C})(A + C) = [(A + \bar{B})C](A + C) \\ &= (A + \bar{B})(AC + CC) = (A + \bar{B})(AC + C) = AAC + AC + A\bar{B}C + \bar{B}C \\ &= AC + AC + \bar{B}C(A + 1) = AC + \bar{B}C(1) = AC + \bar{B}C \\ &= (A + \bar{B})C \end{aligned}$$






Input/Output Waveforms

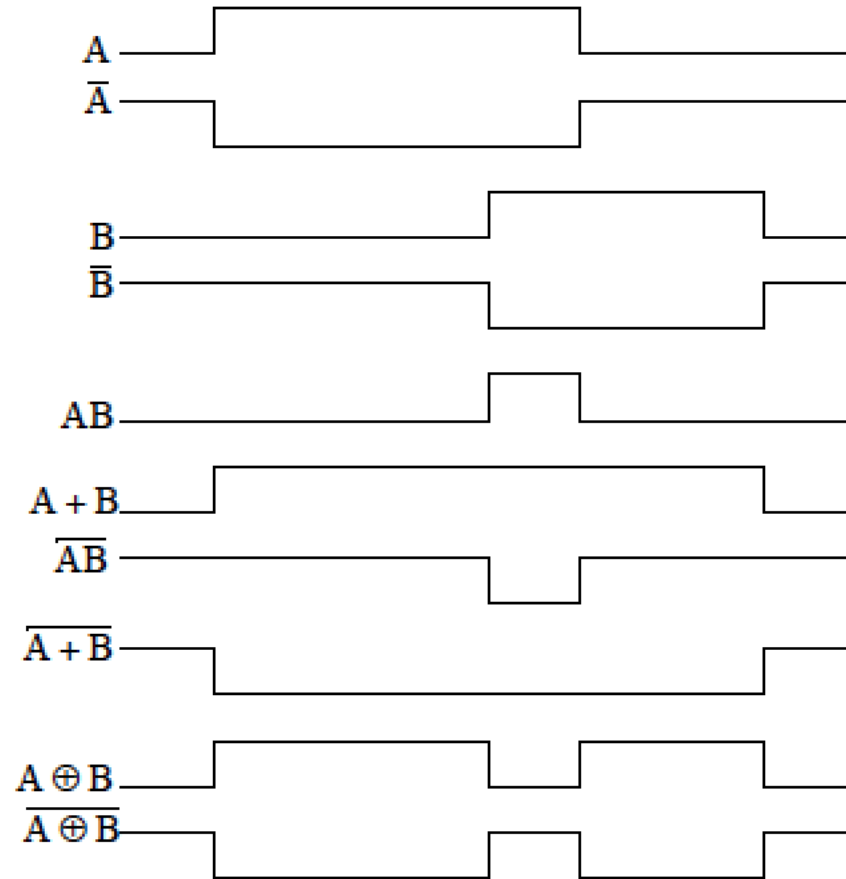

Input/Output Waveforms

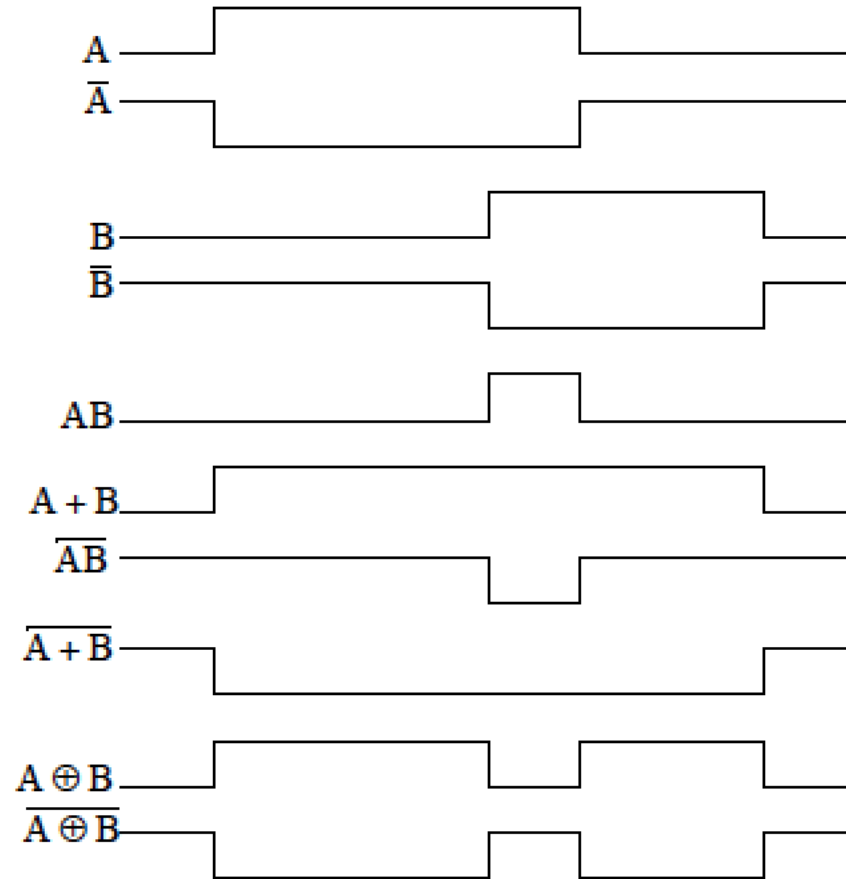

Ex.

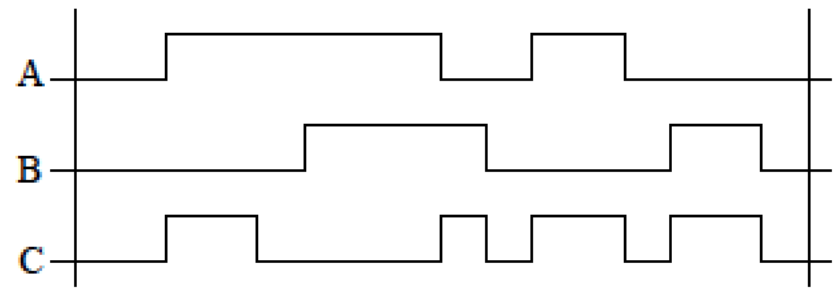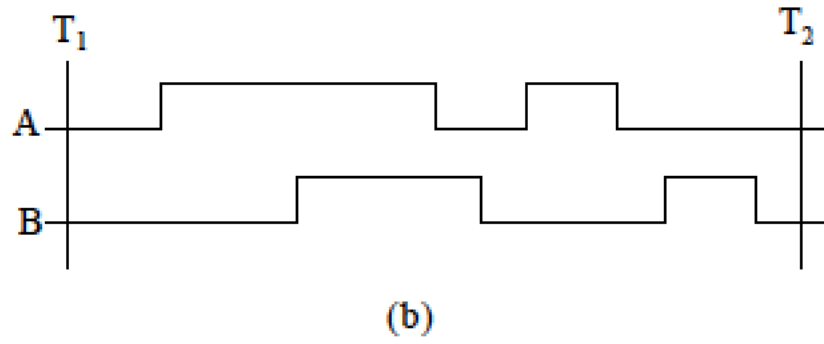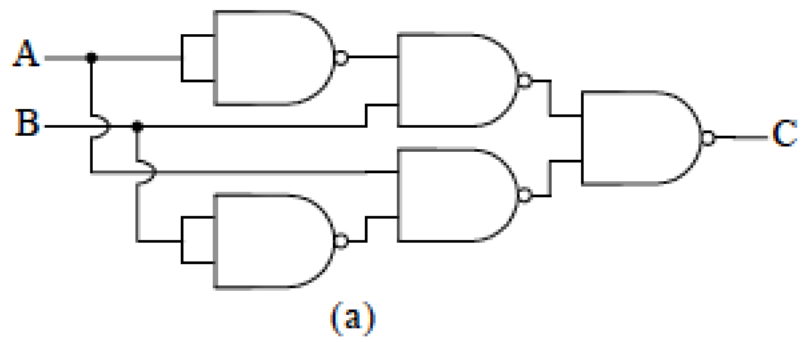

Ref.

(Required Text)

- Steven T. Karris .(2005). Digital Circuit Analysis and Design with an Introduction to CPLDs and FPGAs: Orchard Publications.