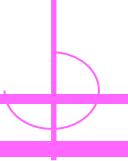




Faculty of Industrial Technology

Suan Sunandha Rajabhat University




Software and Systems Engineering


CPE3202

Pornpawit Boonsrimuang


Cascade interconnection of systems

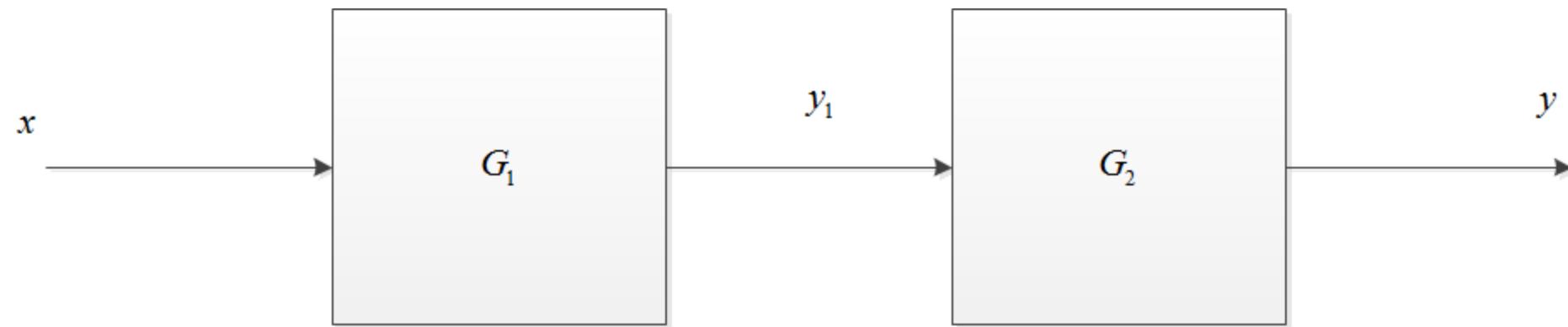


Parallel interconnection of systems

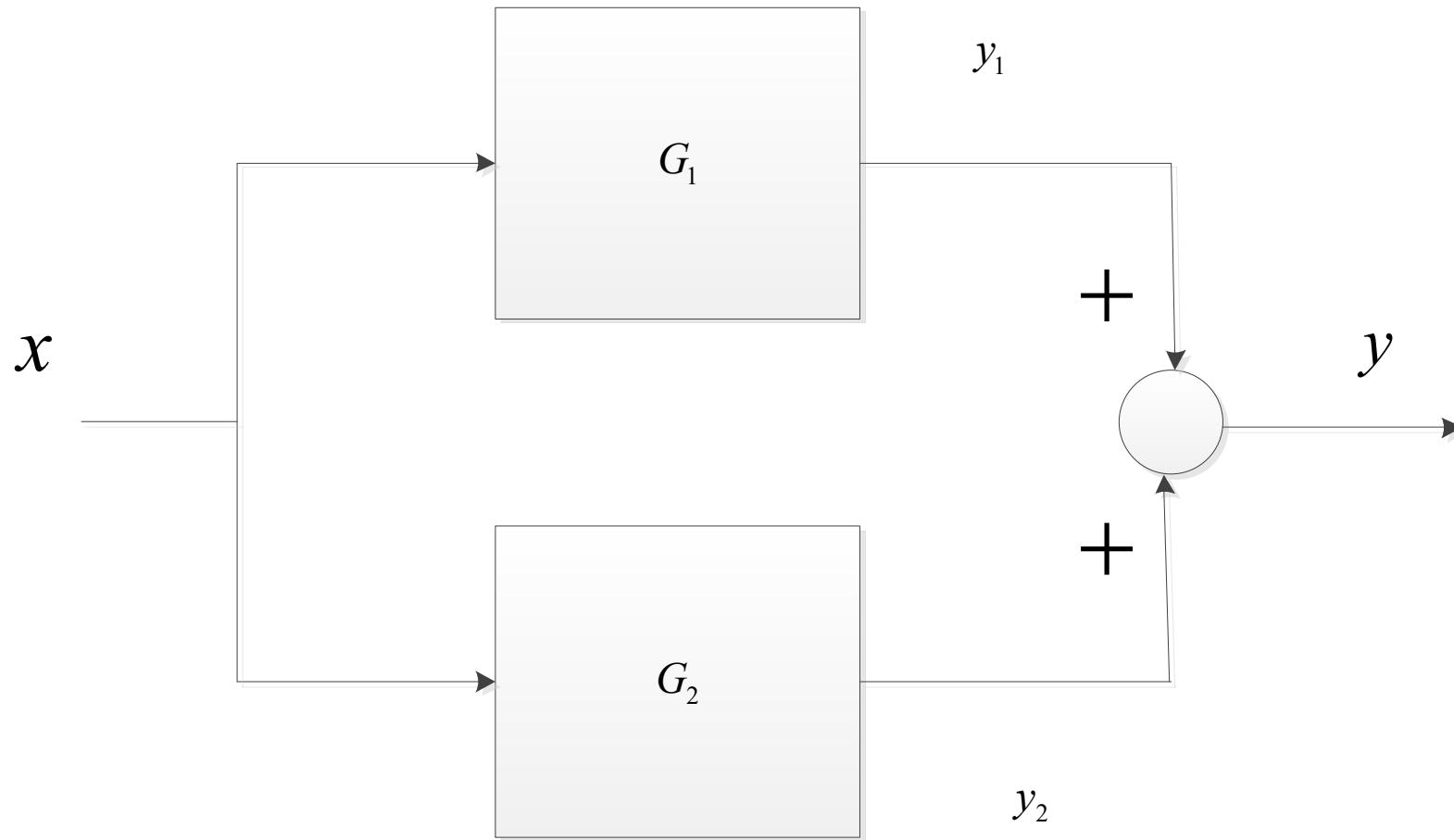


Feedback interconnection of systems

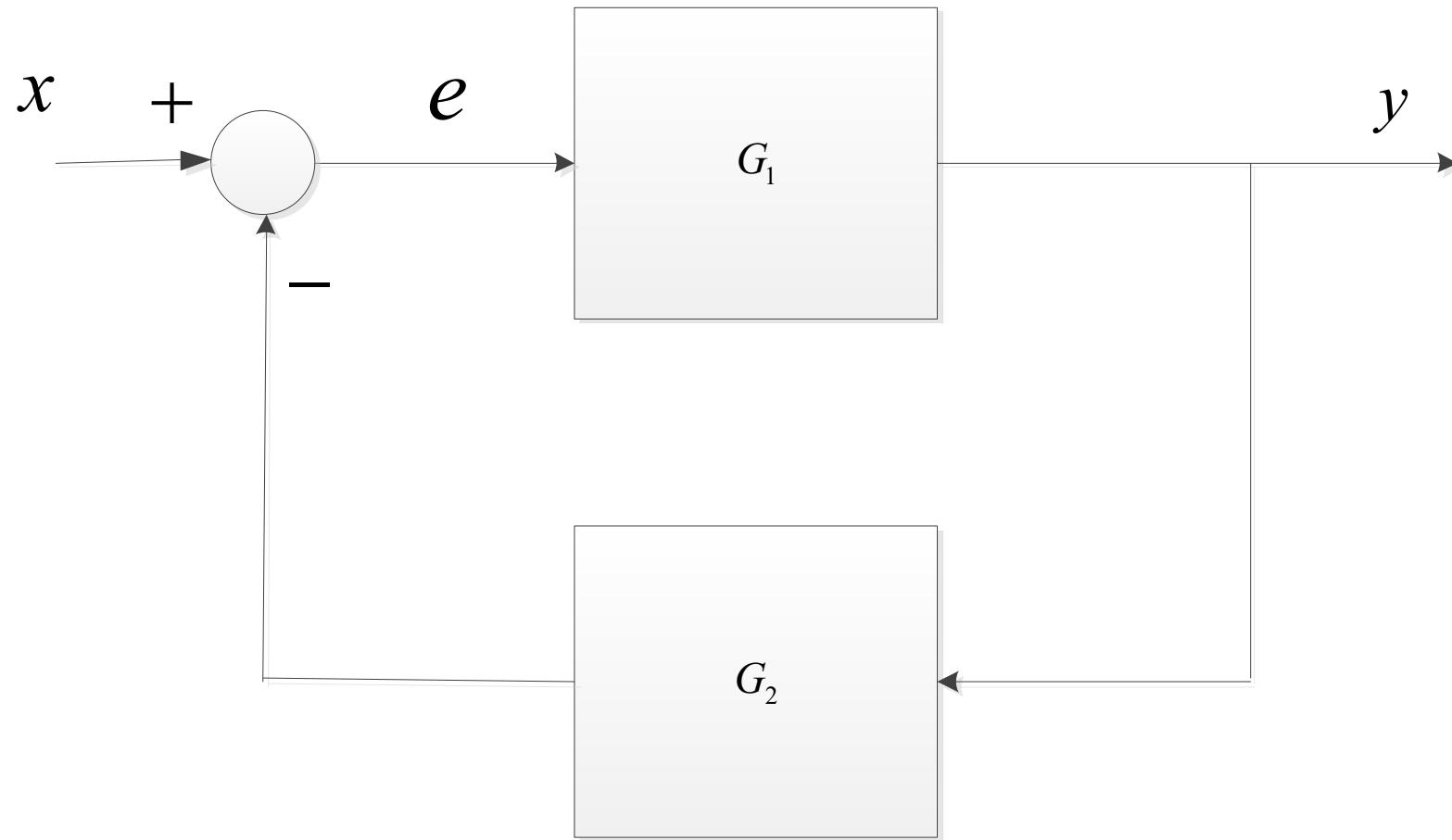

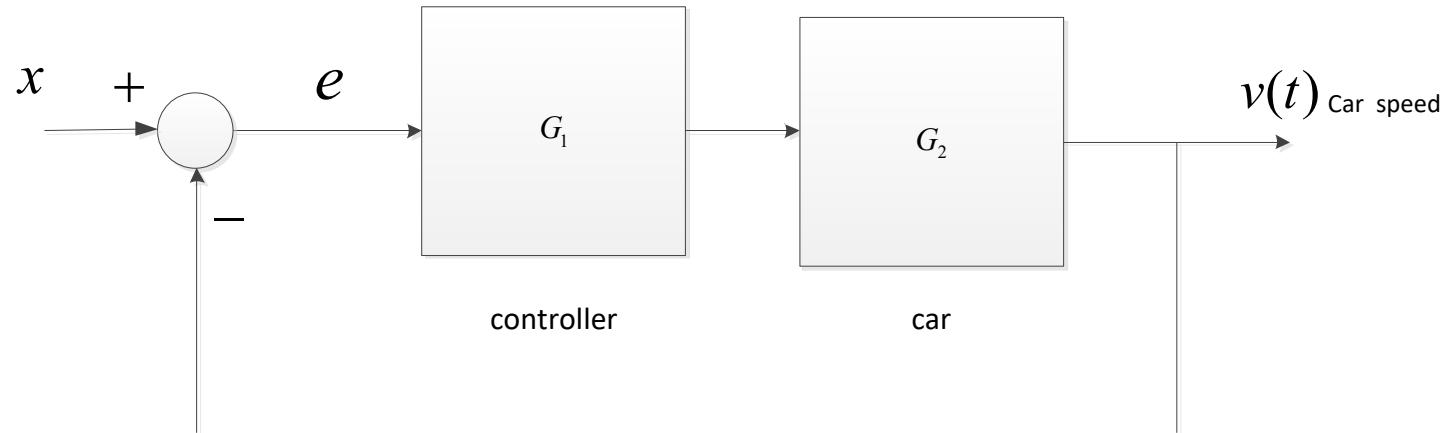Feedback interconnection of a car cruise control systems





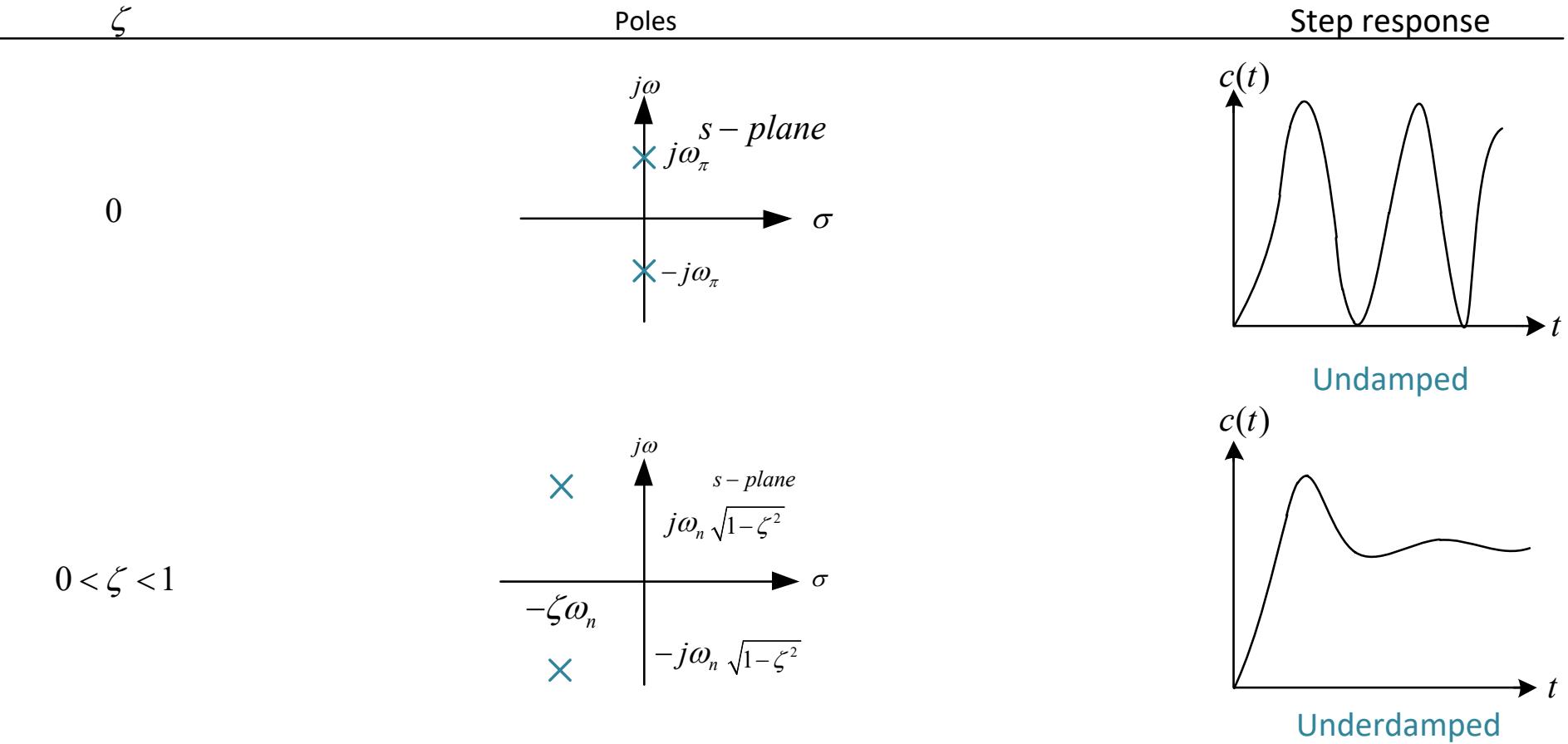Second-order response as a function of damping ratio





Second-order response as a function of damping ratio

$$\zeta = 1$$

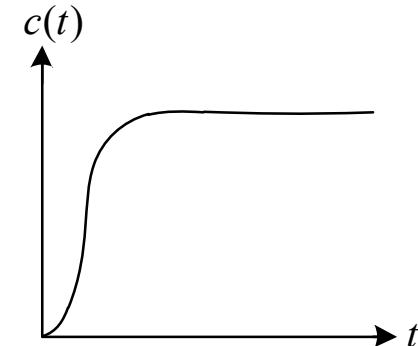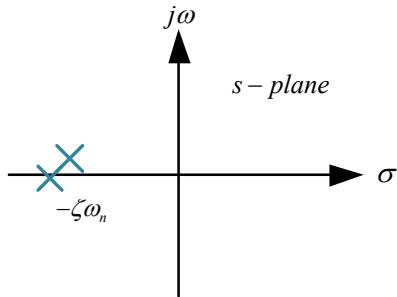


Critically damped

$$\zeta > 1$$

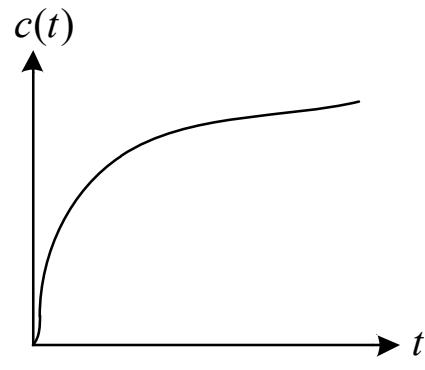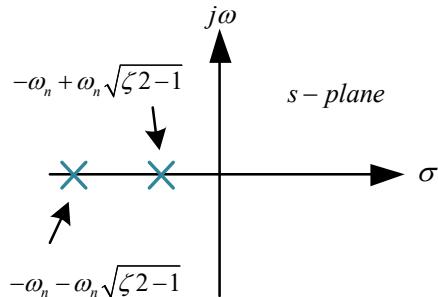


Overdamped

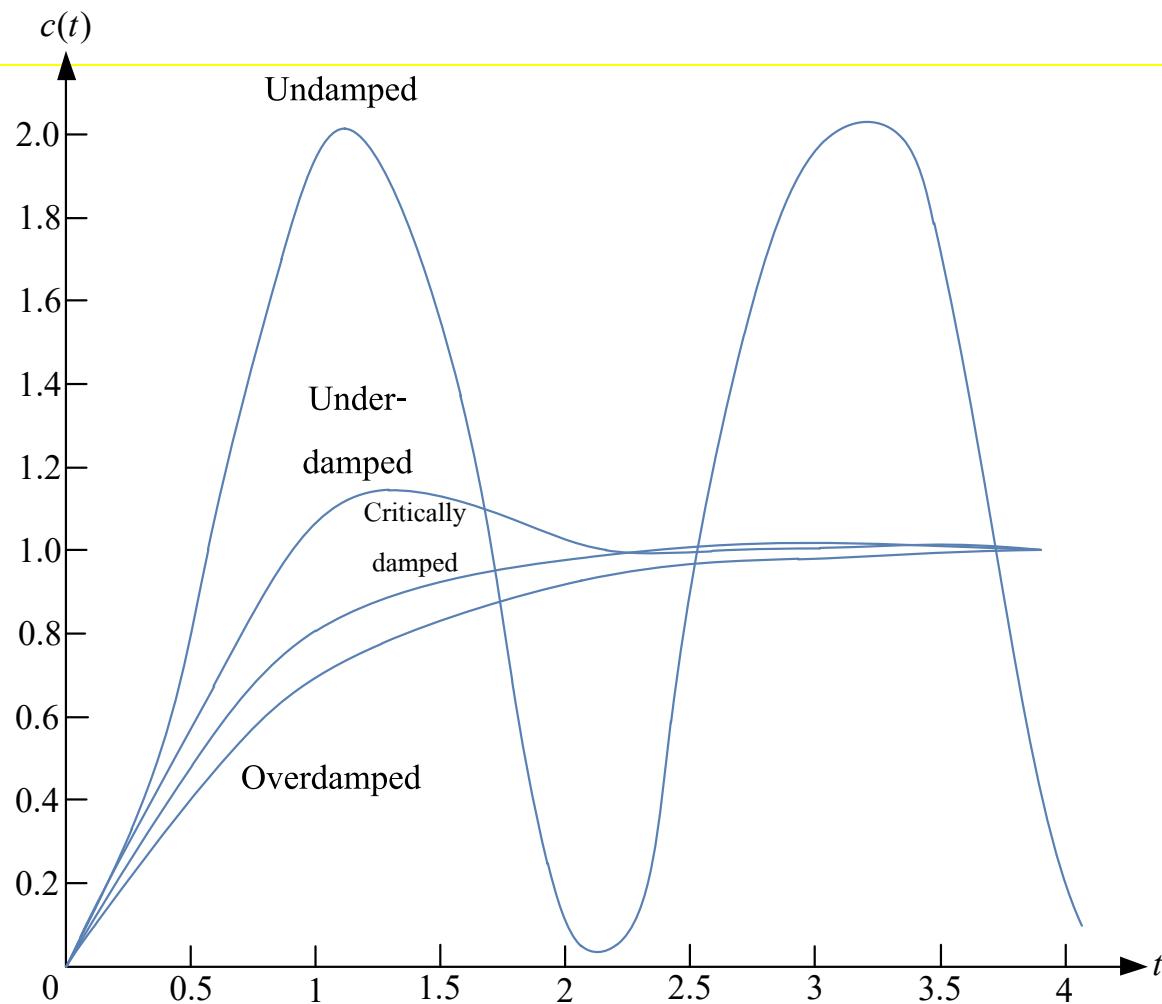Step responses for second-order system damping cases




Ex.

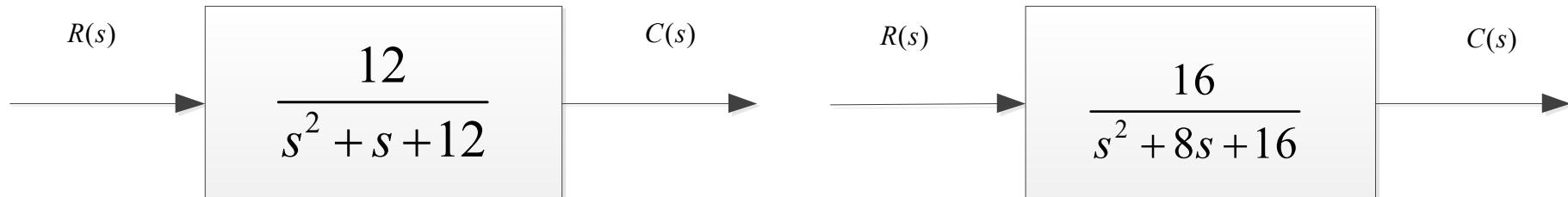

(a)


(b)

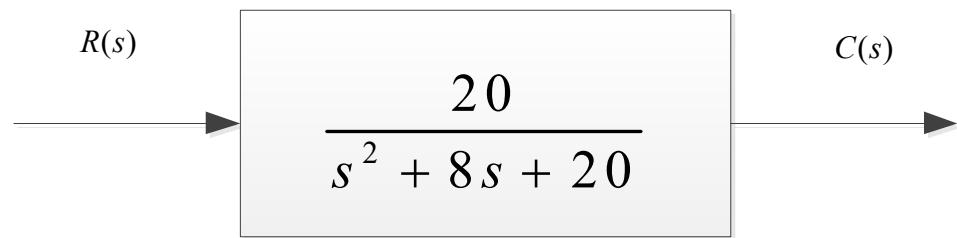


(c)

Ex.




$$c(\omega_n t)$$

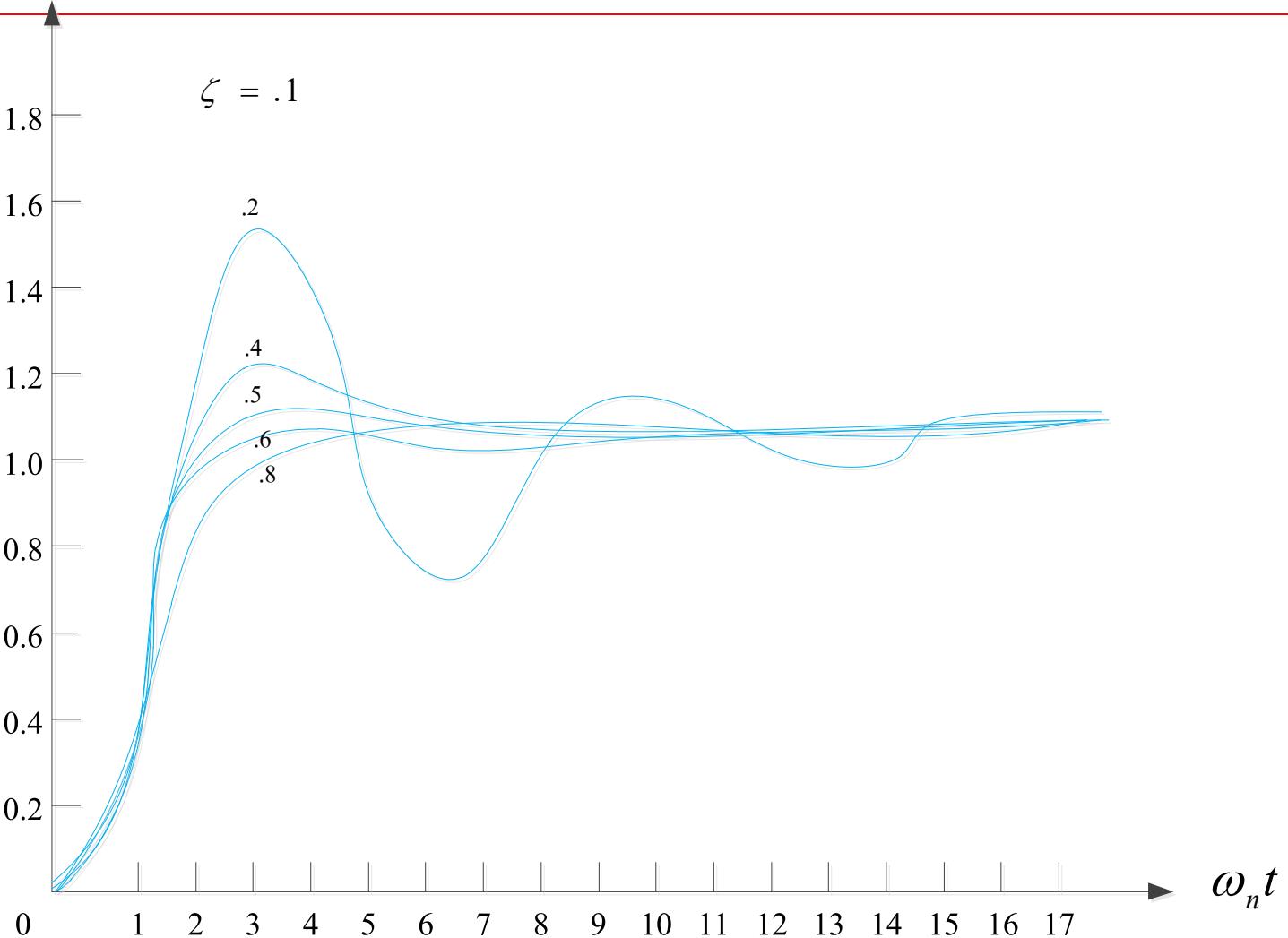




Ex.

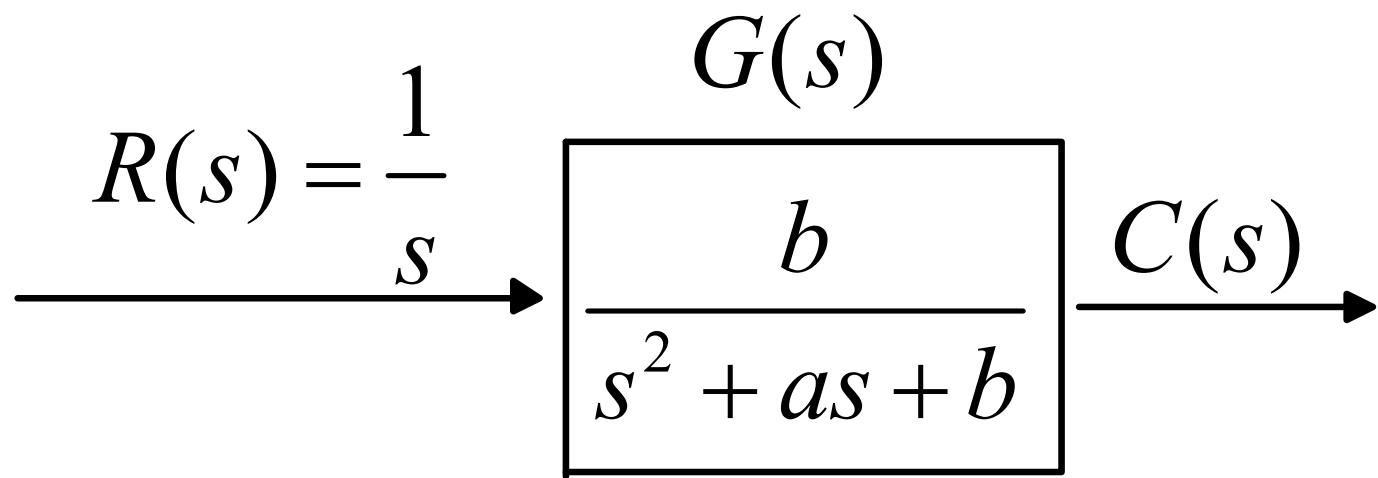




Ex.

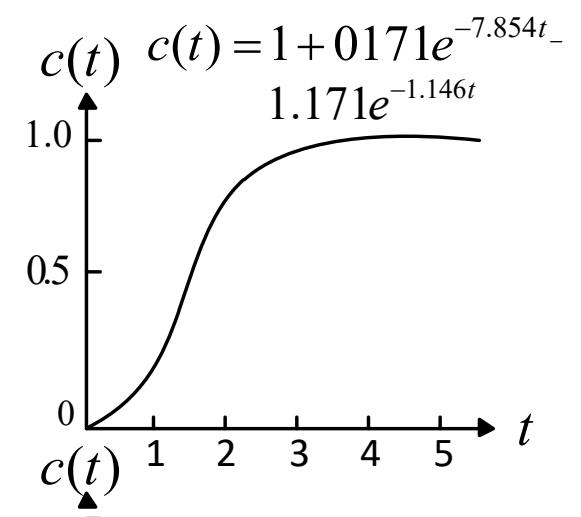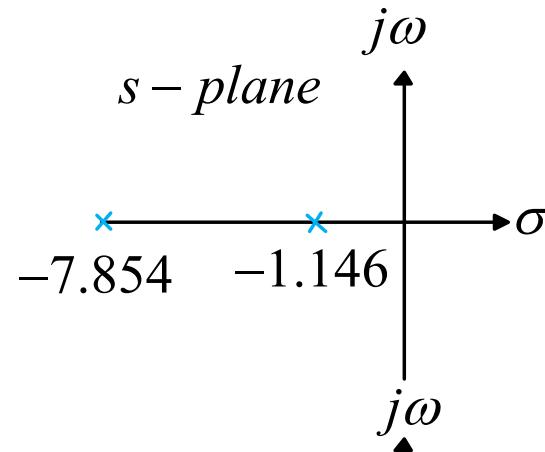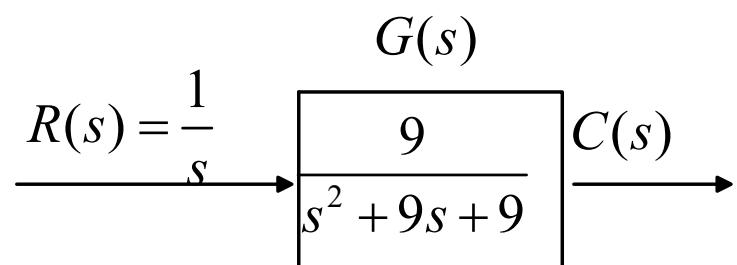




Ex.

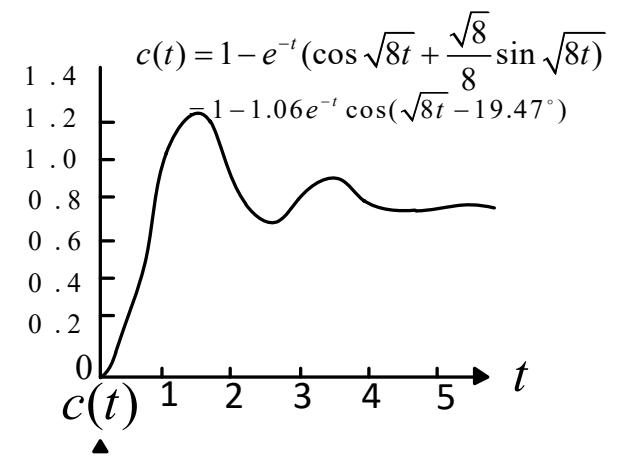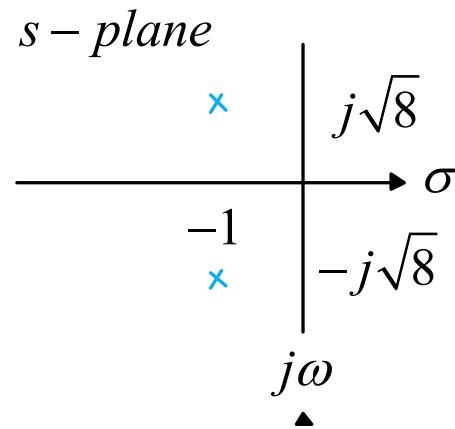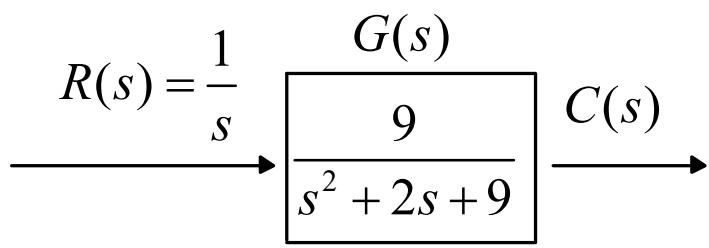



Ex.

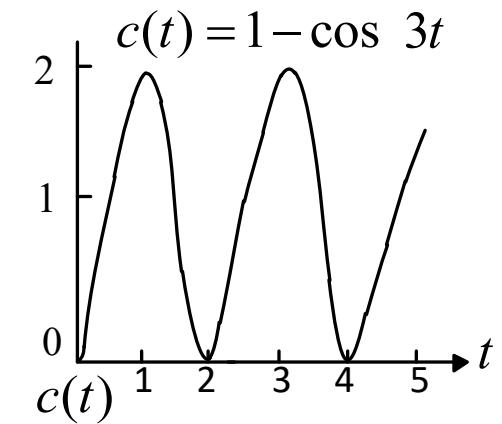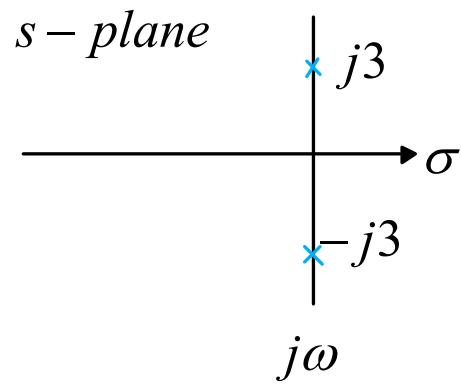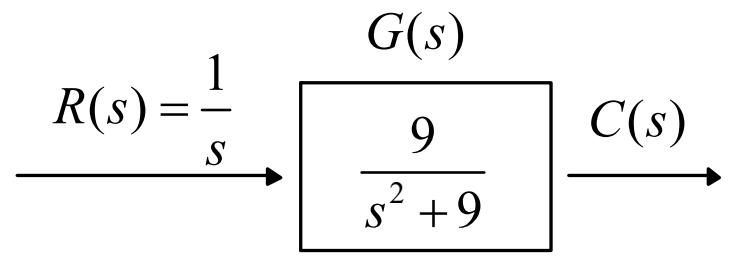


Ex.

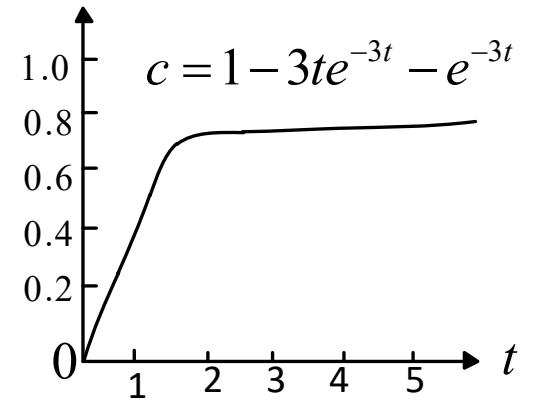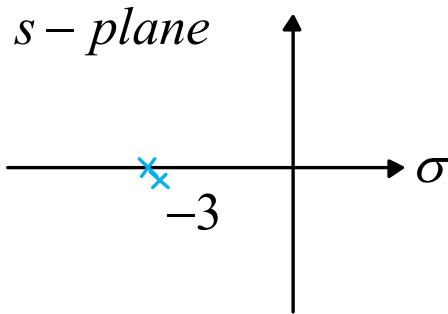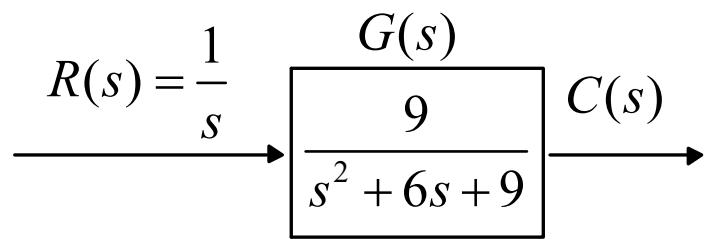


Ex. RC Circuit & Amp.

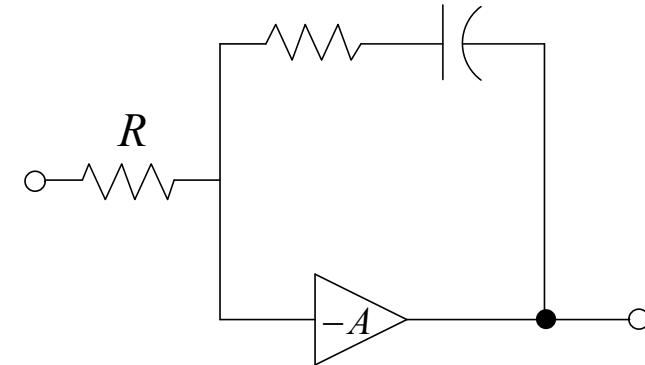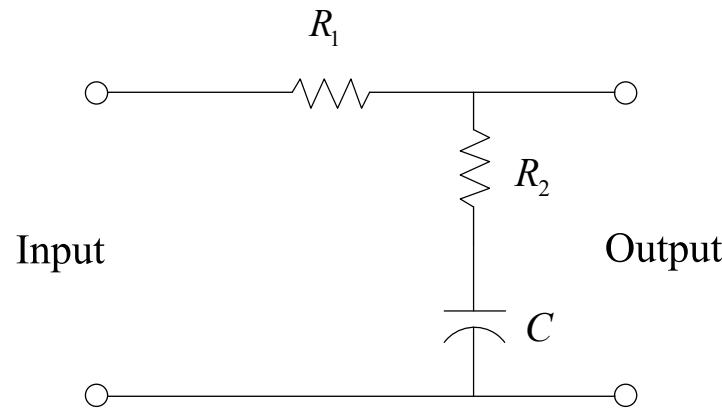


Ex. Feedback

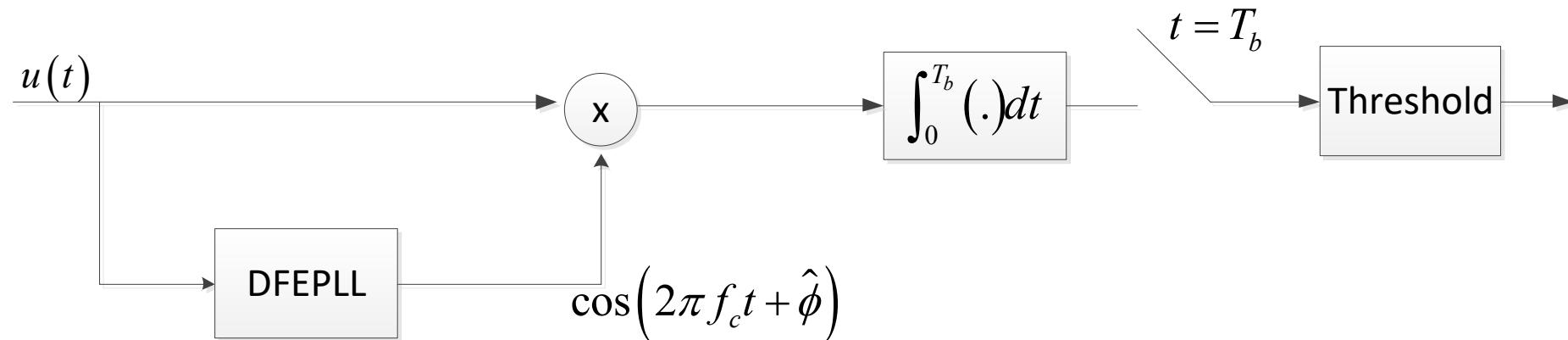


Ex. Feedback

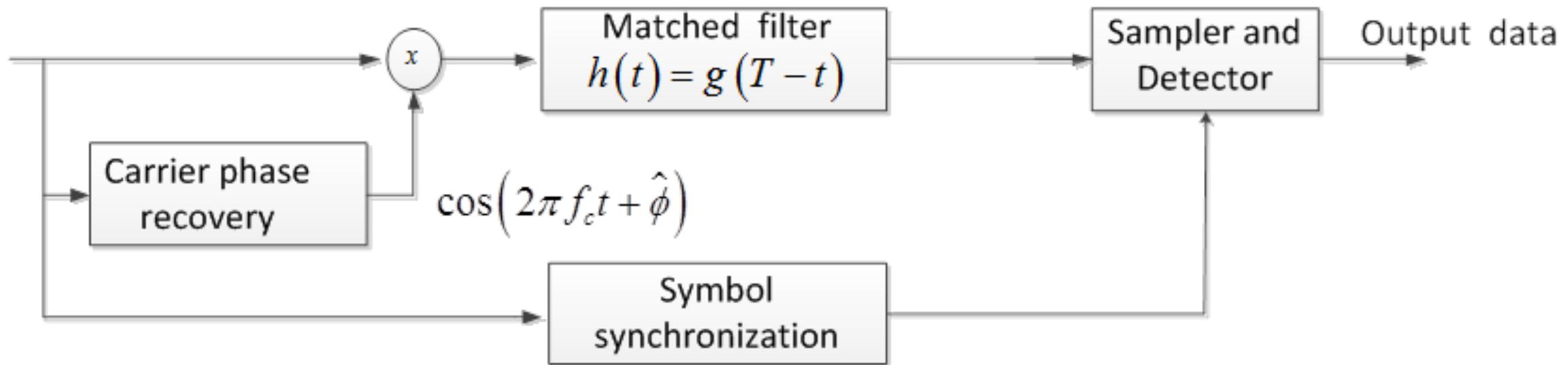

Ex. VCO Block

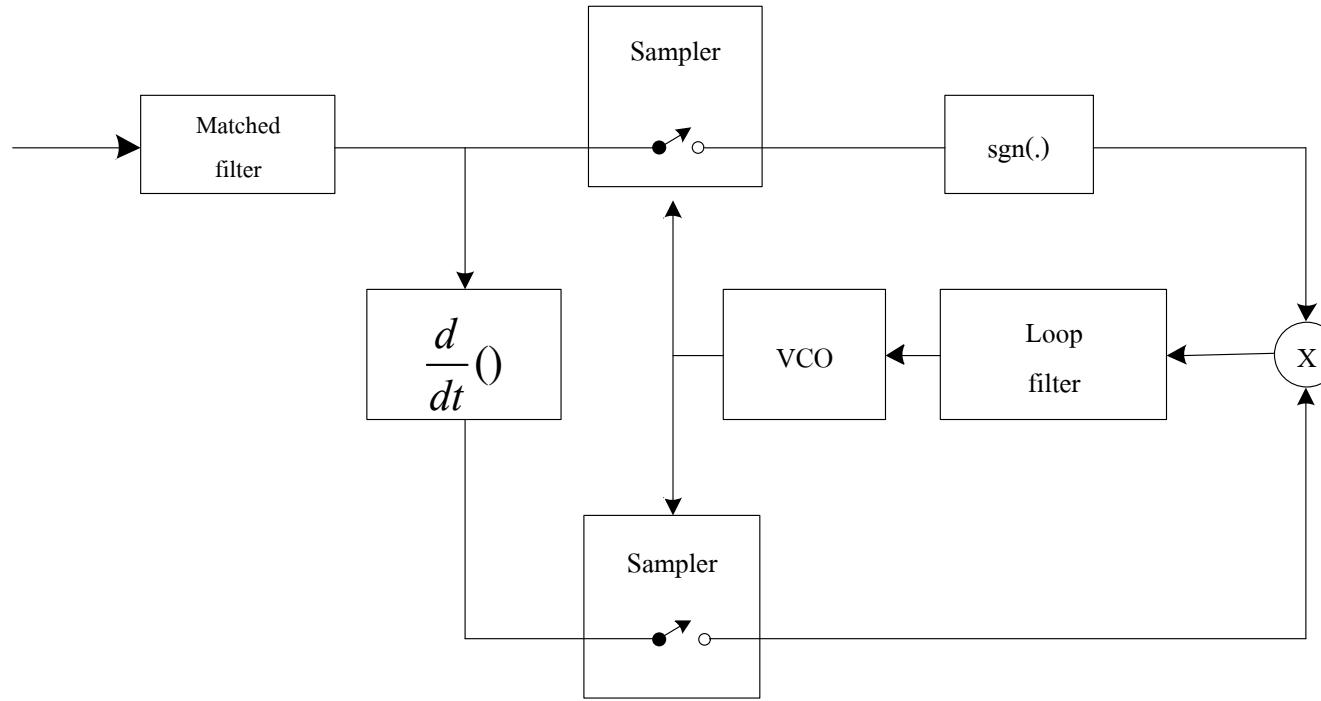

Ex. Serial to Parallel data

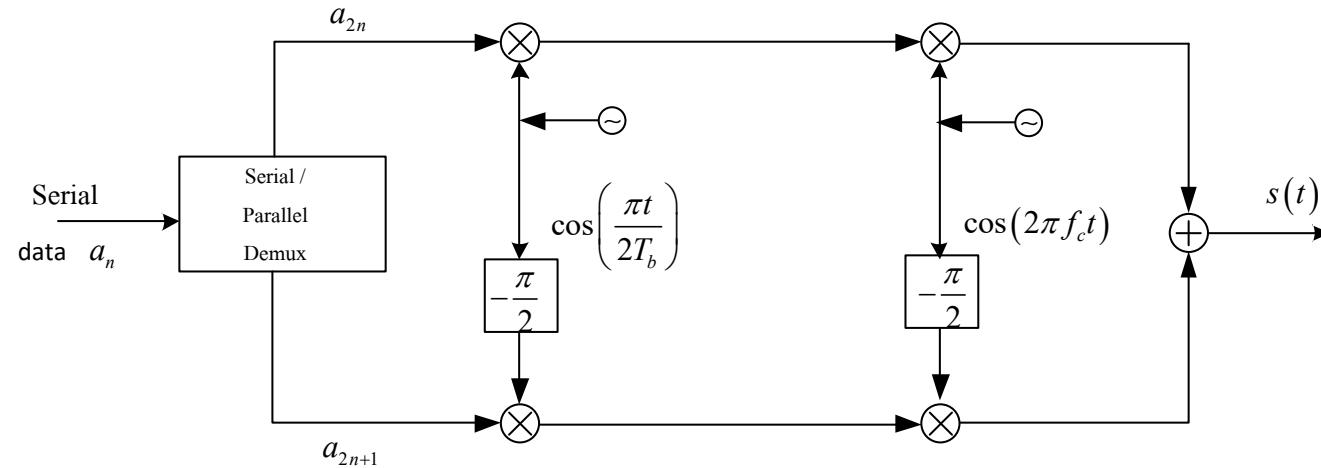

Ex. Serial to Parallel data

